

20p	}	Business
		Test-papers (1-2)
40p	Partial	10 T
		15 A ₁
		15 A ₂
40p	- Final	10 T
		15 A ₁
		15 A ₂

§ 1. Direct Current Circuits

Methods of solving DC circuits

Thereminus

Elements & topology

Kirchoff 1 & 2

Vaschy 1 & 2

Th → Equivalences series, parallel, Δ -*

Th of nonconservation
superposition
reciprocity

Meth. of 1) eg. Transf.

2) Kirchoff system of equations

3) Loop currents

4) Potential at nodes

§ 2. AC - circuits

Variable Sinusoidal

Variable Sources

Elements of the circuit R, L, C

Parallel / Series Structures

Complex Analysis of the AC circuits

Complex Power
 Circuits with Coupled Coils (self/mutual)
 3 phase AC circuits

§ 3. Analysis of non-sinusoidal (periodic time-var) circuits

→ Decomposing on harmonics DC+AC power

§ 4. Transient state

Direct Method
 Laplace Method

Introduction

Topology
 Elements of the circuits

Nodes N


Branches B

Loops L

- N represents the connection of minimum 3 branches
- B = the direct connection between 2 nodes
- L = a close path starting from one node & ending to the same node without crossing twice any branch


Elements < passive
 active

Passive (receptors)

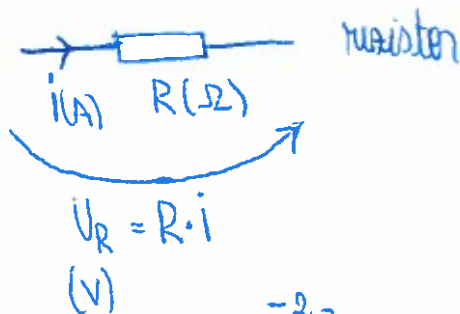

Active elements (generators)

• Voltage source

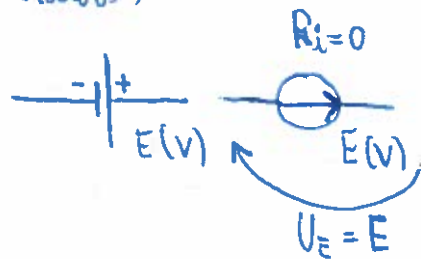

• Current source





G = conductance (S)

$$G = \frac{1}{R}$$

Series & Parallel connection of passive elements

SERIES:

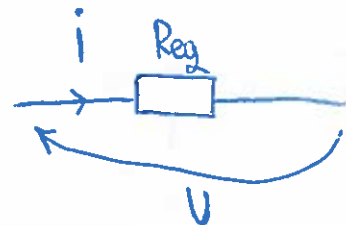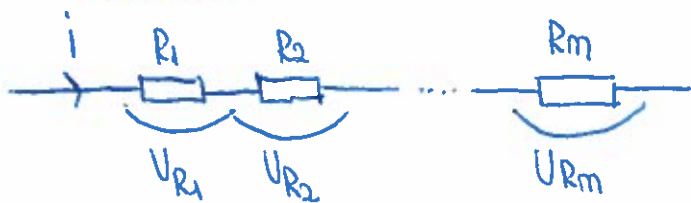

$$U = R_{eq} \cdot i$$

$$U = U_{R1} + U_{R2} + \dots + U_{Rm}$$

$$= R_1 \cdot i + R_2 \cdot i + \dots + R_m \cdot i$$

$$= i \cdot (R_1 + R_2 + \dots + R_m)$$

$$R_{eq} = \sum_{k=1}^m R_k$$

Voltage divider



④

$$U_{R1} = R_1 \cdot \frac{U}{R_{eq}} = \frac{R_1}{R_{eq}} \cdot U = \frac{R_1}{\sum_{k=1}^m R_k} \cdot U$$

$$U_{Rk} = \frac{R_k}{\sum_{h=1}^m R_h} \cdot U$$

formula

Parallel connection

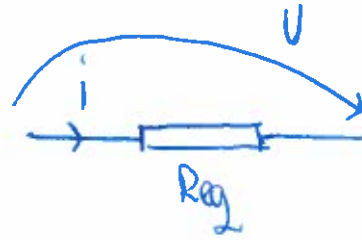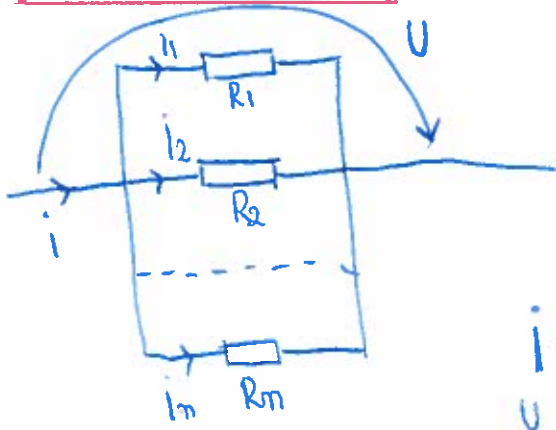


$$i = i_1 + i_2 + \dots + i_m$$
$$\frac{U}{R_{eq}} = \frac{U}{R_1} + \frac{U}{R_2} + \dots + \frac{U}{R_m}$$

$$R_{eq} = \frac{1}{\sum_{k=1}^m \frac{1}{R_k}}$$

Current divider

$$I_1 = \frac{U}{R_1} = \frac{i \cdot R_{eq}}{R_1} = \frac{i}{R_1} \cdot \frac{1}{\sum \frac{1}{R_k}} \Rightarrow$$
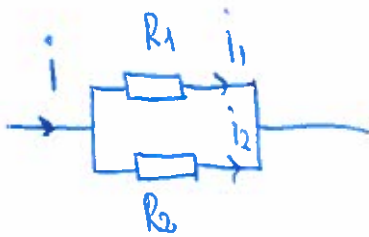
$$I_k = i \cdot \frac{1}{R_k \cdot \sum_{k=1}^m \frac{1}{R_k}} \quad \text{formula}$$




$$U = R_1 \cdot i_1$$

$$U = R_2 \cdot i_2 = i \cdot \frac{R_1 R_2}{R_1 + R_2}$$


$$i_2 = \frac{i R_1 R_2}{R_2 (R_1 + R_2)} = \frac{i R_1}{R_1 + R_2}$$

$$I_1 = \frac{i R_1 R_2}{R_1 (R_1 + R_2)} = \frac{i R_2}{R_1 + R_2}$$

Ohm's Law

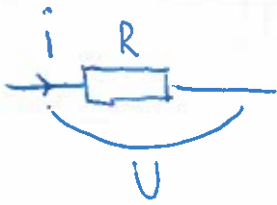

$$U = R \cdot i \quad | : R$$

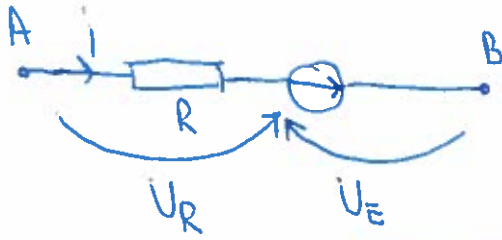

$$U = U_R - U_E = R \cdot i - E \quad | : R$$

$$U_{BA} = U_E - U_R = E - R \cdot i$$



$$\frac{U}{R} = i \Rightarrow \boxed{i = G \cdot U} \quad \star$$

$$U \cdot \frac{1}{R} = i - \frac{E}{R}$$

★

$$\boxed{GU = i - GE}$$

Theorem of equivalent transformation ⑦

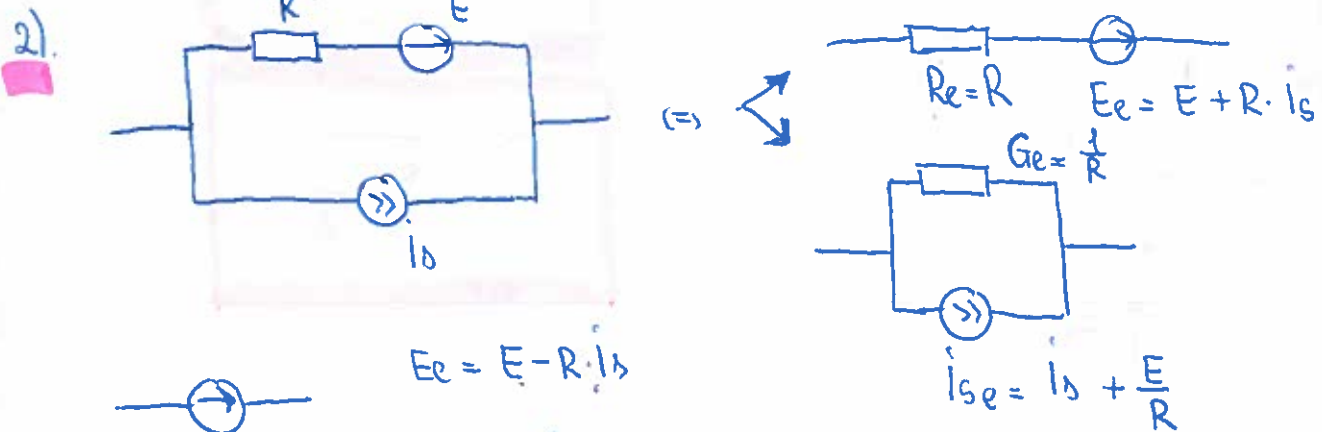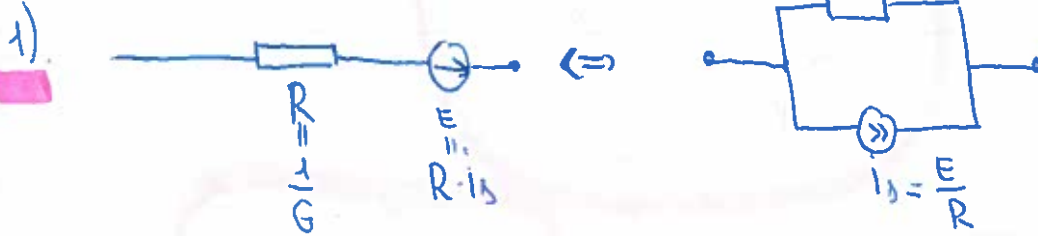


$$E_e = E - R \cdot I_s$$

$$E_e = R \cdot I_s - E$$





5)
a)

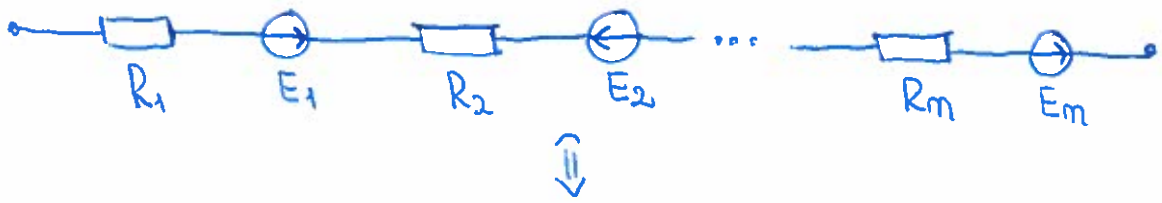

$$R_e = \sum_{k=1}^m R_k$$

$$E = \sum_{k=1}^m E_k$$



b)

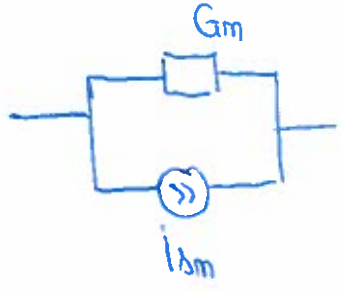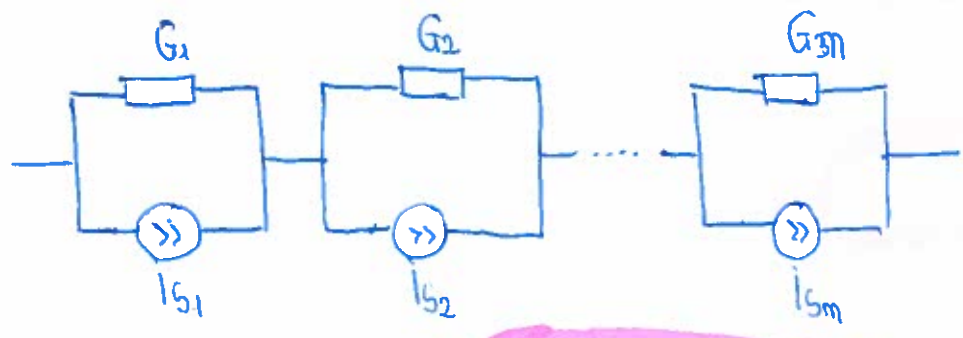

$$I_{GK} = \frac{\sum R_k \cdot I_{SK}}{\sum R_k}$$

$$G_K = \frac{1}{\sum \frac{1}{G_k}}$$


4) a)

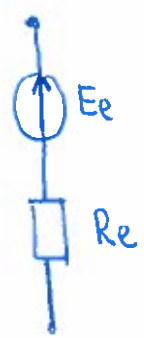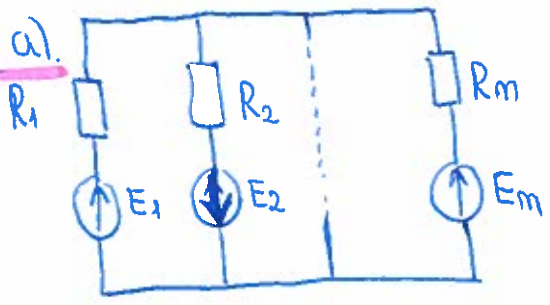

$$E_e = \frac{\sum E_k G_k}{\sum G_k}$$


$$R_e = \frac{1}{\sum_{k=1}^m \frac{1}{R_k}}$$

4 b).

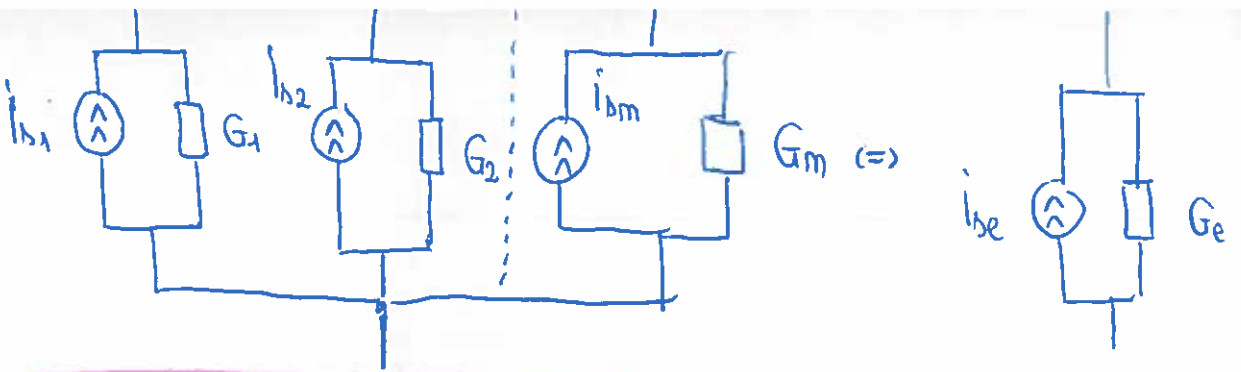

$$G_e = \sum G_h$$

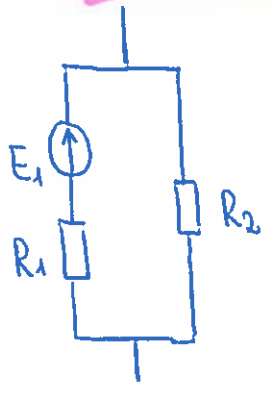
$$i_{se} = \sum_{h=1}^m i_{sh} \quad \text{alg}$$




$$R_e = \frac{R_1 R_2}{R_1 + R_2}$$

$$E_e = \frac{E_1}{\frac{1}{R_1} + \frac{1}{R_2}} + 0 = \frac{E_1 R_2}{R_1 + R_2}$$

application

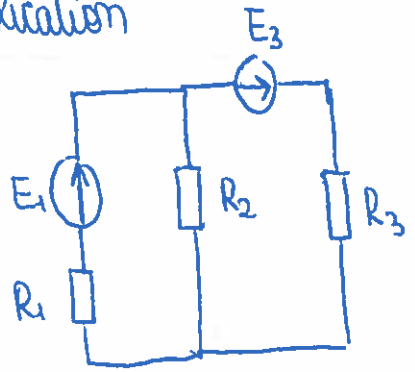


R (Ω)	i (A)	E (V)
R ₁ = 3		E ₁ = 36
R ₂ = 6		
R ₃ = 6		E ₃ = 16

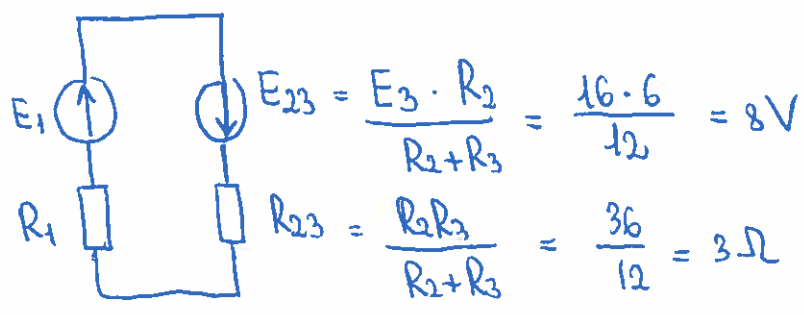

$$E_{23} = \frac{E_3 \cdot R_2}{R_2 + R_3} = \frac{16 \cdot 6}{12} = 8V$$
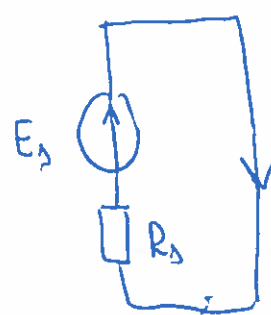
$$R_{23} = \frac{R_2 R_3}{R_2 + R_3} = \frac{36}{12} = 3\Omega$$



$$E_s = E_1 + E_{23} = 36 + 8 = 44V$$

$$R_s = R_1 + R_{23} = 3 + 3 = 6\Omega$$

$$I_1 = \frac{E_s}{R_s} = \frac{44}{6} = 7$$



1
2
3
100