

BAZE CURS 9

27-11-2016

bc:

- Kirchoff Theorems ① & ② ✓
- Vorschr. Theoremen ① & ② ✓
- Eg. generators < voltage (Thiemann) ✓
current (Norton) ✓
- Voltage divider (series conn) ✓
- Current divider (parallel conn) ✓
- The $\star - \Delta$ theorem passive ⑥ ✓ C₃
- Th. of eq. transformation (series / parallel ; current sources / voltage) ✓
- Thorem of power conservation ⑧ ✓
- Thorem of the maximum power transfer ⑨ ✓
- System of eq. { Potential of Node ⑩ ✓ C₄, C₅
Loop Current }

AC:


- The equations of the elements ① G
- The complex transf. for sources ②
- The thorem of conservation for complex power ③
- } R → Z
G → Y

- bc problem:
- { to solve using any kind of meth. litur + num.
 - to express the voltage between 2 nodes (Ohm's Law)
 - to find the eg. generator with respect to 2 nodes (Thiemann + Norton)
 - Power Balance

- AC circuit : {
- 2 voltage source without coupled coils
 - < 3 branches, 1 source, with coupled coil

+ Power Balance
+ Kirchoff eq in time domain
+ to represent the phases of the currents and one phaser for a reactive element

APL ①

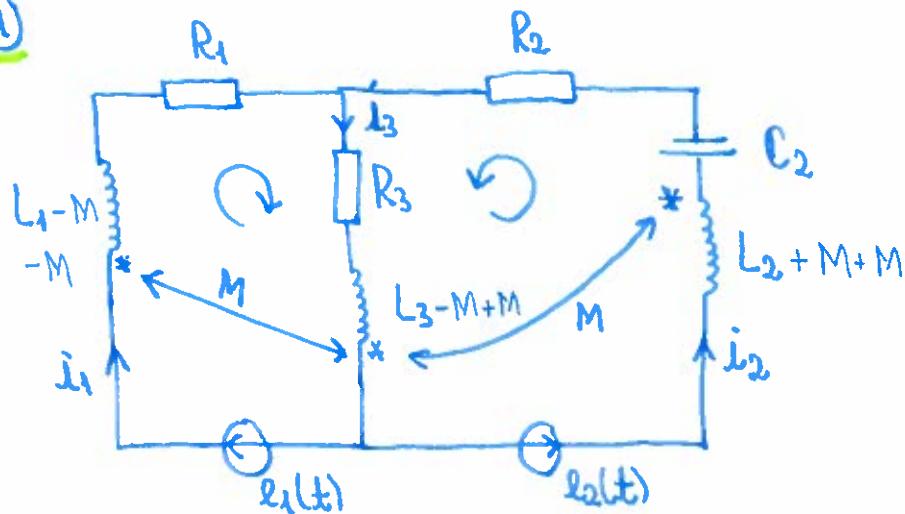

$$e_1(t) = 60 \sin(100t + \pi/4)$$

$$e_2(t) = 35\sqrt{2} \sin(100t + \pi/2)$$

$$R_1 = 20\Omega \quad R_2 = 25\Omega \quad R_3 = 5\Omega$$

$$L_1 = L_3 = 100 \text{ mH} \quad L_2 = M = 50 \text{ mH}$$

$$C_2 = 0.5 \text{ mF}$$

$$i_3 = i_1 + i_2$$

$$e_1 = R_1 i_1 + L_1 \frac{di_1}{dt} - M \frac{di_3}{dt} + \underbrace{R_3 i_3}_{\text{II } R_3} + \underbrace{L_3 \frac{di_2}{dt}}_{\text{II } L_3} - M \frac{di_1}{dt} + M \frac{di_2}{dt}$$


$$e_2 = R_2 i_2 + \underbrace{\frac{1}{C_2} \int i_2 dt}_{\text{II } C_2} + \underbrace{L_2 \frac{di_2}{dt}}_{\text{II } L_2} + M \frac{di_3}{dt} + \underbrace{L_3 \frac{di_3}{dt}}_{\text{II } L_3} - M \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$+ R_3 i_3$$

$$\left\{ \begin{array}{l} L_1' = L_1 - 2M = 100 - 100 = 0 \\ L_3' = L_3 - M + M = L_3 = 100 \text{ mH} \\ L_2' = L_2 + 2M = 50 + 100 = 150 \text{ mH} \end{array} \right.$$

Homework: literally all methods + solve 1 + P.B check

APL 2

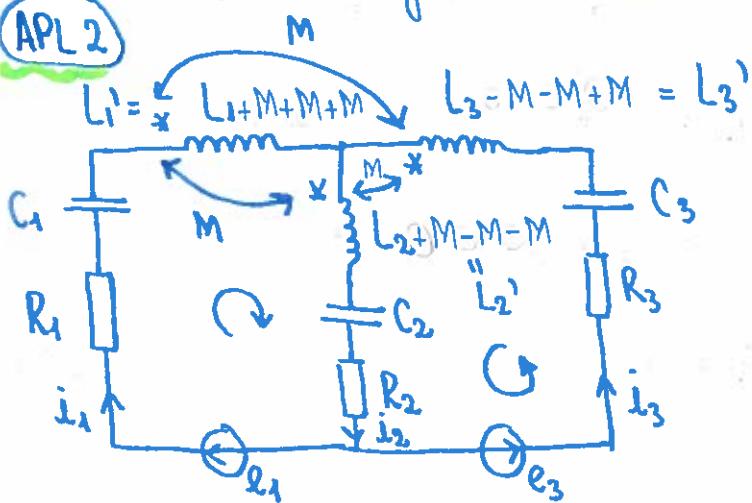

$$e_1(t) = 240 \sin(1000t)$$

$$e_3(t) = 60 \sin(1000t + \frac{\pi}{2})$$

$$R_1 = R_2 = R_3 = 10 \Omega \quad L_1 = 15 \text{ mH}$$

$$L_2 = 35 \text{ mH} \quad L_3 = M = 5 \text{ mH}$$

$$C_1 = 100 \mu F \quad C_2 = C_3 = 50 \mu F$$

$$i_2 = i_1 + i_3$$


$$e_1 = i_1 R_1 + \frac{1}{C_1} \int i_1 dt + \underbrace{L_1 \frac{di_1}{dt} - M \frac{di_3}{dt}}_{\mu L_1} + M \frac{di_2}{dt} + \frac{1}{C_2} \int i_2 dt + R_2 i_2 + \underbrace{L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} - M \frac{di_3}{dt}}_{\mu L_2}$$

$$e_2 = R_3 i_3 + \frac{1}{C_3} \int i_3 dt + L_3 \frac{di_3}{dt} - M \frac{di_2}{dt} - M \frac{di_1}{dt} + \underbrace{\mu L_2 + \mu C_2 + \mu R_2}_{\mu L_3}$$

$$L_1' = L_1 + 3M = 30 \text{ mH}$$

$$L_2' = L_2 - M = 30 \text{ mH}$$

$$L_3' = L_3 - M = 0$$

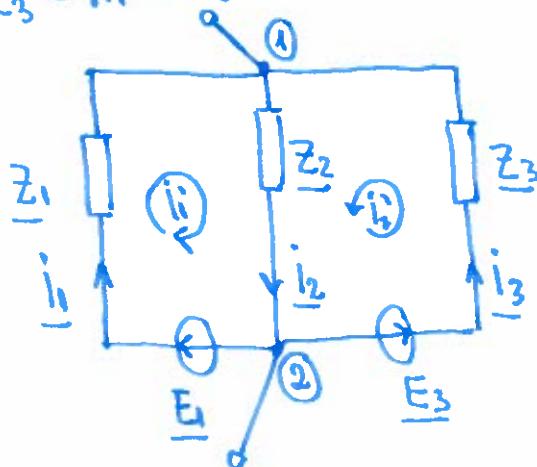

$$\underline{Z}_1 = R_1 + j(\omega L_1' + \frac{1}{\omega C_1}) \\ = 10 + j(30 - 10) = 10(1+2j)$$

$$\underline{Z}_2 = R_2 + j(\omega L_2' + \frac{1}{\omega C_2}) \\ = 10 + j(30 - 20) = 10(1+j)$$

$$\underline{Z}_3 = R_3 + j(\omega L_3' - \frac{1}{\omega C_3}) = 10(1-2j)$$

$$E_1 = 120\sqrt{2} e^{j0^\circ} = 120\sqrt{2}$$

$$E_3 = 30\sqrt{2} e^{j\frac{\pi}{2}} = 30\sqrt{2}j$$



$$\underline{Z}_{eq} = \frac{1}{\frac{1}{\underline{Z}_1} + \frac{1}{\underline{Z}_2} + \frac{1}{\underline{Z}_3}} = \frac{1}{Y_1 + Y_2 + Y_3}$$

$$1-j \cdot \frac{1}{\frac{1}{10(1+2j)} + \frac{1}{10(1+j)} + \frac{1}{10(1-2j)}} =$$

$$\frac{10}{\frac{1-2j}{5} + \frac{1-j}{2} + \frac{1+2j}{5}} = \frac{10}{\frac{2}{5} \frac{2}{5} \frac{1}{2}} = \frac{100}{9-5j} = \frac{100(9+5j)}{106}$$

$$E_{eq} = \frac{E_1 Y_1 + 0 \cdot Y_2 + E_3 \cdot Y_3}{Y_1 + Y_2 + Y_3}$$

$$\left\{ \begin{array}{l} I_1 + I_3 = I_2 \\ E_1 = Z_1 I_1 + Z_2 I_2 \\ E_3 = Z_3 I_3 + Z_2 I_2 \end{array} \right. \quad \text{N} \quad \left\{ \begin{array}{l} V_2 = 0 \\ Y_{11} V_1 = Y_{DC1} \\ Y_{11} = Y_1 + Y_2 + Y_3 \\ I_{DC1} = I_1 \cdot Y_1 + I_3 \cdot Y_3 \end{array} \right.$$

$$V_1 - V_2 = \begin{cases} E_1 - Z_1 I_1 \\ E_3 - Z_3 I_3 \\ Z_2 I_2 \end{cases}$$

loop Current

$$Z_{11} I_1' + Z_{12} I_2' = E_1'$$

$$Z_{21} I_1' + Z_{22} I_2' = E_2'$$

$$Z_{11} = Z_1 + Z_2$$

$$Z_{22} = Z_2 + Z_3$$

$$Z_{12} = Z_{21} = +Z_2$$

$$E_1' = E_1$$

$$E_2' = E_3$$

$$\left\{ \begin{array}{l} I_1 = I_1' \\ I_3 = I_2' \\ I_2 = I_1' + I_2' \end{array} \right.$$

$$S_{gm} = E_1 \cdot I_1^* + E_3 \cdot I_3^*$$

$$S_{max} = Z_1 \cdot I_1^2 + Z_2 \cdot I_2^2 + Z_3 \cdot I_3^2$$

$$P = \operatorname{Re}\{S\} \text{ (W)}$$

$$Q = \operatorname{Im}\{S\} \text{ VAR}$$