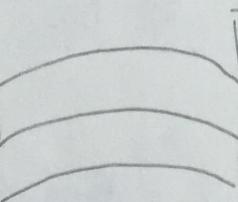


Three phase AC circuit

3 phase system
of generators
(voltage sources)



3 phase
Reactor


$m_1(t), m_2(t), m_3(t)$
symmetrical one

$$M_1 = M_2 = M_3$$

120° (between them)

symmetrical
system


direct (DSS)
reverse (ISS)

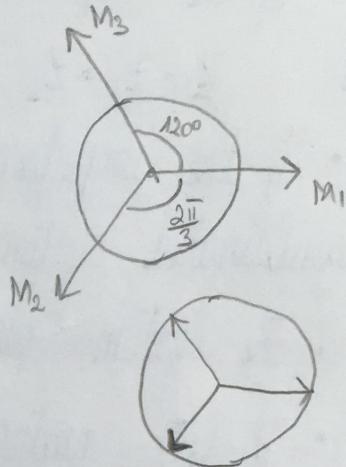Theorem of sum = 0

In any system of three phase symmetrical, the 3 quantities involved in the system have the sum equal to 0.

$$m_1 + m_2 + m_3 = 0$$

$$\begin{aligned} & M_1 \exp[j\theta] + M_2 \exp[-j\frac{2\pi}{3}] + M_3 \exp[j\frac{2\pi}{3}] = \\ & = M + M \left[\cos\left(-\frac{2\pi}{3}\right) + j \sin\left(-\frac{2\pi}{3}\right) \right] + M \cdot \left[\cos\frac{2\pi}{3} + j \sin\frac{2\pi}{3} \right] \\ & = M \left(1 + \left(-\frac{1}{2}\right) - \frac{\sqrt{3}}{2}j - \frac{1}{2} + \frac{\sqrt{3}}{2}j \right) = 0 \end{aligned}$$

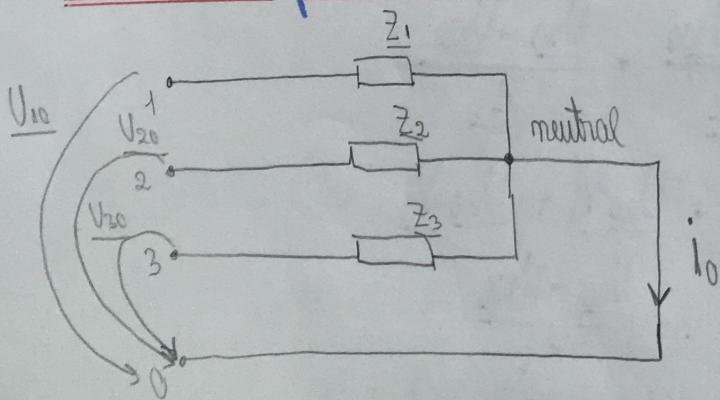Star three phase AC circuit

$$\begin{aligned} \underline{U_{10}} &= \underline{0} \\ \underline{U_{20}} &= -\frac{2\pi}{3} \\ \underline{U_{30}} &= +\frac{2\pi}{3} \end{aligned}$$

no specification

$$\left\{ \begin{array}{l} u_{10}(t) = U_{10}\sqrt{2} \sin(\omega t + \phi) \\ u_{20}(t) = U_{20}\sqrt{2} \sin(\omega t + \phi - \frac{2\pi}{3}) \\ u_{30}(t) = U_{30}\sqrt{2} \sin(\omega t + \phi + \frac{2\pi}{3}) \end{array} \right. \quad \text{for } \Delta S S$$

• If the impedances are equal, then we have equilibrated system $\underline{Z}_1 = \underline{Z}_2 = \underline{Z}_3$

• If the impedances are not equal, then we have non-equilibrated system.

• The system can be with or without neutral conductor

• If (\exists) neutral conductor (N.C.) we can have $\begin{cases} \text{with } \underline{Z}_0 \\ \text{without } \underline{Z}_0 \end{cases}$

$$\left\{ \begin{array}{l} i_0 = i_1 + i_2 + i_3 \\ U_{10} = \underline{U}_{1N} + \underline{U}_{NO} \\ U_{20} = \underline{U}_{2N} + \underline{U}_{NO} \\ U_{30} = \underline{U}_{3N} + \underline{U}_{NO} \end{array} \right. \quad \left\{ \begin{array}{l} \underline{U}_{1N} = \underline{Z}_1 i_1 \\ \underline{U}_{2N} = \underline{Z}_2 i_2 \\ \underline{U}_{3N} = \underline{Z}_3 i_3 \\ \underline{U}_{NO} = \underline{Z}_0 i_0 \end{array} \right.$$

Theorem of displacement of the neutral mode

$$\Rightarrow \underline{U}_{NO} = \frac{\underline{U}_{10} Y_1 + \underline{U}_{20} Y_2 + \underline{U}_{30} Y_3}{Y_0 + Y_1 + Y_2 + Y_3} \quad Y_0 = \frac{1}{\underline{Z}_0} \quad Y_R = \frac{1}{\underline{Z}_R}$$

$$\text{Quesn: } \frac{\underline{U}_{NO}}{\underline{Z}_0} = \frac{\underline{U}_{10} - \underline{U}_{NO}}{\underline{Z}_1} + \frac{\underline{U}_{20} - \underline{U}_{NO}}{\underline{Z}_2} + \frac{\underline{U}_{30} - \underline{U}_{NO}}{\underline{Z}_3}$$

$$\underline{U}_{NO} (Y_0 + Y_1 + Y_2 + Y_3) = \underline{U}_{10} Y_1 + \underline{U}_{20} Y_2 + \underline{U}_{30} Y_3$$

$$i_1 = \frac{\underline{U}_{10} - \underline{U}_{NO}}{\underline{Z}_1}$$

$$i_2 = \frac{\underline{U}_{20} - \underline{U}_{NO}}{\underline{Z}_2}$$

$$i_3 = \frac{\underline{U}_{30} - \underline{U}_{NO}}{\underline{Z}_3}$$

$$i_0 = \frac{\underline{U}_{NO}}{\underline{Z}_0}$$


Particular case $(\underline{Z}) \underline{Z}_0$

$$\Rightarrow \underline{V}_{N0} = 0 \Rightarrow \underline{V}_{10} = \underline{V}_{1N} = \underline{Z}_1 \underline{i}_1 \quad \underline{i}_1 = \frac{\underline{V}_{10}}{\underline{Z}_1} \quad \underline{i}_R = \frac{\underline{V}_{R0}}{\underline{Z}_R}$$

$$\underline{S}_{rec} = \underline{V}_{1N} \underline{i}_1^* + \underline{V}_{2N} \underline{i}_2^* + \underline{V}_{3N} \underline{i}_3^* + \underline{V}_{N0} \underline{i}_0^*$$

$$\underline{S}_{gen} = \underline{V}_{10} \underline{i}_1^* + \underline{V}_{20} \underline{i}_2^* + \underline{V}_{30} \underline{i}_3^*$$

Triangle three phase AC circuit

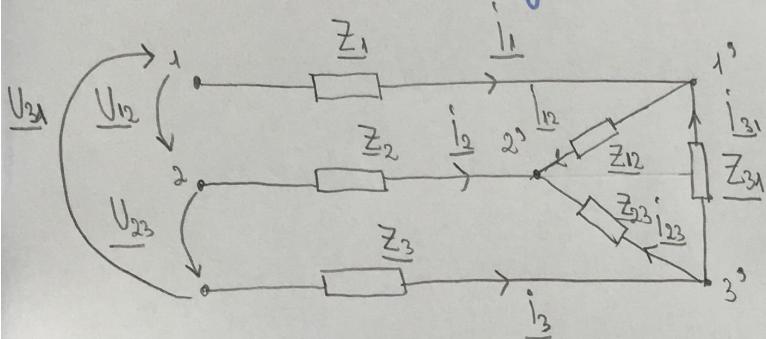

- symmetrical system

$$\underline{U}_{12} + \underline{U}_{23} + \underline{U}_{31} = 0$$

$$u_{12}(t) = U_{12}\sqrt{2} \sin(\omega t + \phi)$$

$$u_{23}(t) = U_{23}\sqrt{2} \sin(\omega t + \phi \pm \frac{2\pi}{3}) \quad \text{DSS}/i_{ss}$$

$$u_{31}(t) = U_{31}\sqrt{2} \sin(\omega t + \phi \pm \frac{2\pi}{3}) \quad \text{DSS}/i_{ss}$$

The most common phase: $\underline{Z}_1 = \underline{Z}_2 = \underline{Z}_3 = 0$

$$K_I : \begin{cases} \underline{i}_1 = \underline{i}_{12} - \underline{i}_{31} \\ \underline{i}_2 = \underline{i}_{23} - \underline{i}_{12} \\ \underline{i}_3 = \underline{i}_{31} - \underline{i}_{23} \end{cases}$$

$$K_{II} : \begin{cases} \underline{U}_{12} = \underline{Z}_1 \underline{i}_1 + \underline{Z}_{12} \underline{i}_{22} - \underline{Z}_2 \underline{i}_2 \\ \underline{U}_{23} = \underline{Z}_2 \underline{i}_2 + \underline{Z}_{23} \underline{i}_{23} - \underline{Z}_3 \underline{i}_3 \\ \underline{U}_{31} = \underline{Z}_3 \underline{i}_3 + \underline{Z}_{31} \underline{i}_{31} - \underline{Z}_1 \underline{i}_1 \end{cases}$$

For $\underline{Z}_1 = \underline{Z}_2 = \underline{Z}_3$ K_I remains the same

$$K_{II} : \begin{cases} \underline{U}_{12} = \underline{Z}_{12} \underline{i}_{12} \Rightarrow \underline{i}_{12} = \frac{\underline{U}_{12}}{\underline{Z}_{12}} \\ \underline{U}_{23} = \underline{Z}_{23} \underline{i}_{23} \Rightarrow \underline{i}_{23} = \frac{\underline{U}_{23}}{\underline{Z}_{23}} \\ \underline{U}_{31} = \underline{Z}_{31} \underline{i}_{31} \Rightarrow \underline{i}_{31} = \frac{\underline{U}_{31}}{\underline{Z}_{31}} \end{cases}$$