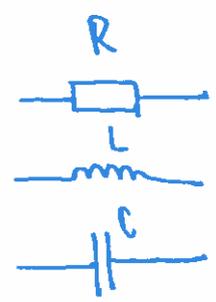


→ sources → periodical functions
harmonics (Fourier analysis)

Th of superposition

DC + (AC) $k = 1, m$
"k0" $\omega \dots k\omega \dots m\omega$




$$e(t), i_s(t) = f(t) = \underbrace{F^{(0)}}_{DC} + \underbrace{f(t)^{(1)}}_{AC} + \dots$$

eg.


$$e_1 = E_1$$

$$e_2 = E_2 + E_2 \sqrt{2} \sin(\omega t) + 2E_2 \sqrt{2} \sin(3\omega t)$$

Being under DC conditions :

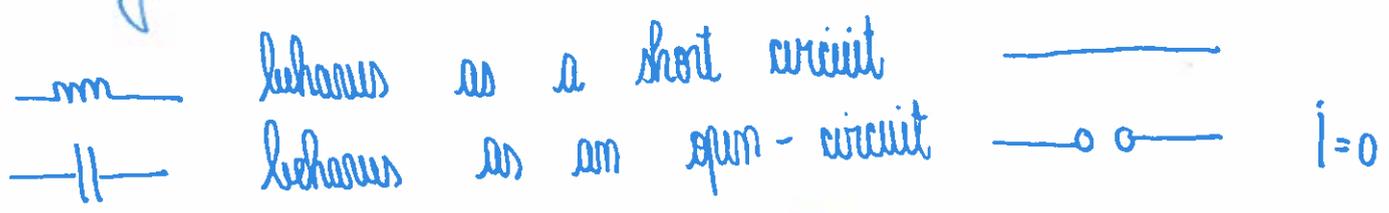

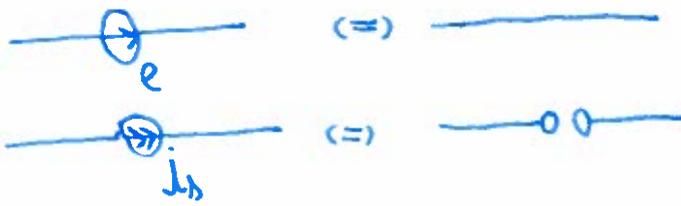On the harmonics, where they don't have components, the voltage sources will be replaced by shortcircuits and the current sources will be replaced by open-circuit.



$$\omega \rightarrow i_1(t) = I_1 \sqrt{2} \sin(\omega t + \phi)$$

Remark:

We pay attention to the direction of the currents in the branches for the respective harmonics

The solution of the circuit with periodic non-sinus. sources (by applying the superposition theory) will be the algebraical sum of the solutions obtained on each separated harmonic.

$$i(t) = i^{(0)} + i(t)^{(1)} + \dots + i(t)^{(m)}$$

In the algebraical sum, we take with + or - the comp. depending on how we have kept or not the initial direction of the current in the branch


$$I = \sqrt{I^{(0)2} + I^{(1)2} + \dots + I^{(m)2}}$$

effective value

P - active
Q - reactive
S - apparent
 $S^2 \neq P^2 + Q^2$

it appears $D = \sqrt{S^2 - (P^2 + Q^2)}$
distortion power

example:


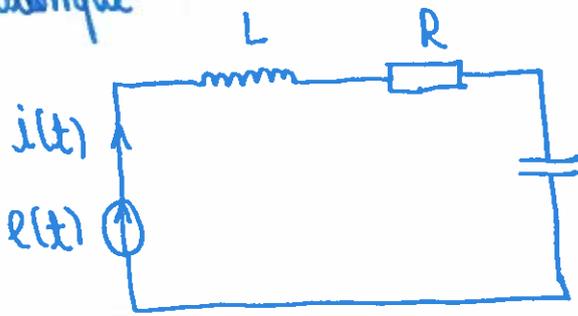


$$R = 24 \Omega \quad \omega L = \frac{1}{\omega C} = 5 \Omega$$

$$e(t) = E + \underbrace{E \sin \omega t}_{e(t)^{(1)}} + \underbrace{4E \sin 5\omega t}_{e(t)^{(2)}}$$


$$E = 48V$$

$$i(t), u_C(t) = ?$$

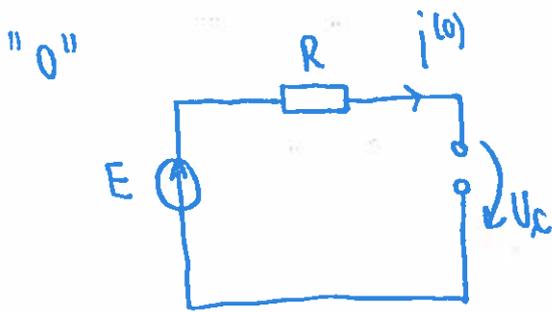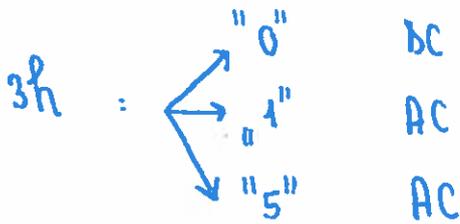

$$i^{(0)} = 0$$

$$u_C^{(0)} = E$$

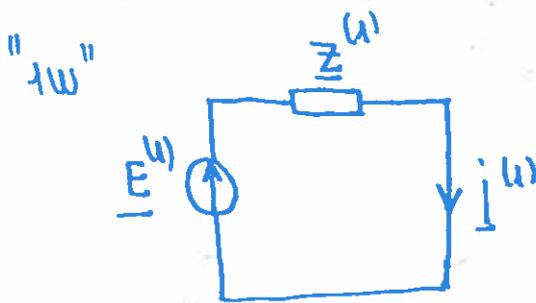

$$\underline{E}^{(1)} = \frac{E\sqrt{2}}{2} e^{j0} = 24\sqrt{2}$$

$$\underline{Z}^{(1)} = R + j(\omega L - \frac{1}{\omega C}) = R$$

if we have series resonance on a AC circuit, we don't have resonance some on the rest of the harmonics

the no of harmonic influences the calculation of the inductive & capacitive impedances in such way that the


inductive reactance increases as many times as the number of harmonics when the capacitive reactance decreases as many times as the number of harmonics.

$$\underline{i}^{(n)} = \frac{\underline{E}^{(n)}}{\underline{Z}^{(n)}} = \frac{24\sqrt{2}}{24} = \sqrt{2} e^{j0} \quad i(t)^{(n)} = 2 \sin \omega t$$

$$\underline{V}_c^{(n)} = \underline{Z}_c^{(n)} \cdot \underline{i}^{(n)} = \frac{-j}{\omega C} \cdot \underline{i}^{(n)} = -5j\sqrt{2} = 5\sqrt{2} (0-j) = 5\sqrt{2} e^{j-\frac{\pi}{2}}$$

$$v_c(t)^{(n)} = 10 \sin(\omega t - \frac{\pi}{2})$$

"5W":

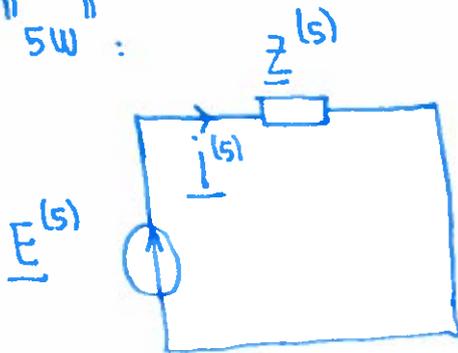

$$\underline{E}^{(s)} = \frac{4E\sqrt{2}}{2} e^{j0} = 96\sqrt{2}$$

$$\underline{Z}^{(s)} = R + j(5\omega L - \frac{1}{5\omega C})$$

$$(5XL - \frac{X_c}{5})$$

$$= 24 + j(5 \cdot 5 - \frac{5}{5}) = 24 + 24j$$

$$\underline{i}^{(s)} = \frac{\underline{E}^{(s)}}{\underline{Z}^{(s)}} = \frac{96\sqrt{2}}{24(1-j)} = \frac{4\sqrt{2}(1-j)}{2} = 4(\frac{\sqrt{2}}{2} - \frac{\sqrt{2}}{2}j) = 4e^{j-\frac{\pi}{4}}$$

$$i(t)^{(s)} = 4\sqrt{2} \sin(5\omega t - \frac{\pi}{4})$$

$$\underline{V}_c^{(s)} = \underline{Z}_c^{(s)} \cdot \underline{i}^{(s)} = -j \frac{1}{5\omega C} \cdot \underline{i}^{(s)} = -j \cdot \frac{4\sqrt{2}}{2} (1-j) = \frac{4\sqrt{2}}{2} (-1-j)$$

$$= 4e^{j\frac{5\pi}{4}}$$

$$v_c(t)^{(s)} = 4\sqrt{2} \sin(5\omega t + \frac{5\pi}{4})$$

$$i(t) = i^{(0)} + i(t)^{(1)} + i(t)^{(5)} = 0 + 2 \sin \omega t + 4\sqrt{2} \sin(5\omega t - \frac{\pi}{4})$$


$$I = \sqrt{i^{(0)2} + i^{(1)2} + i^{(5)2}} = \sqrt{0^2 + (\sqrt{2})^2 + 4^2} = \sqrt{18} \text{ A} = 3\sqrt{2} \text{ A}$$

$$u_C(t) = u_C^{(0)} + u_C^{(1)} + u_C^{(5)}$$

$$= 48 + 10 \sin(\omega t - \frac{5\pi}{2}) + 4\sqrt{2} \sin(5\omega t + \frac{5\pi}{4})$$

$$U_C = \sqrt{U_C^{(0)2} + U_C^{(1)2} + U_C^{(5)2}} = \sqrt{48^2 + (5\sqrt{2})^2 + 4^2} \text{ V}$$

APL 2

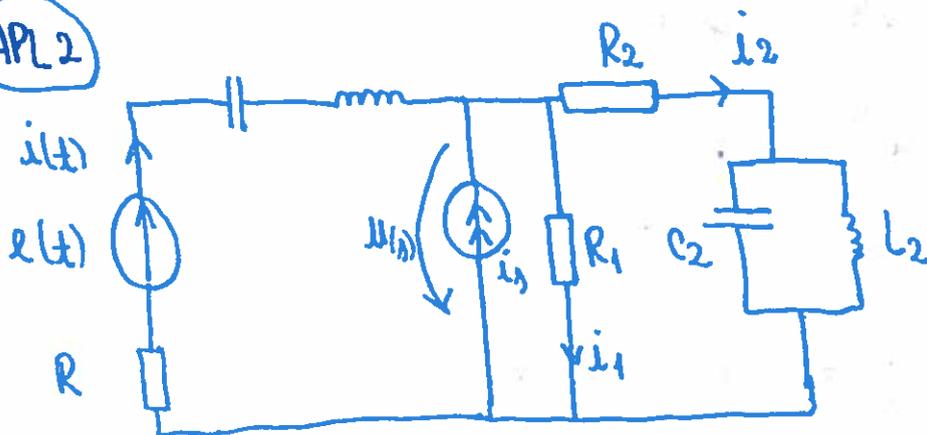

$$R = R_1 = R_2 = 10 \Omega$$

$$L = 8 \text{ mH}$$

$$C = 0.5 \text{ mF}$$



$$L_2 = 50 \text{ mH}$$

$$C_2 = 80 \mu\text{F}$$

$$i_s(t) = \textcircled{2 \text{ A}} \text{ "0" DC}$$

$$e(t) = \underbrace{80}_{\text{"0"}} + \underbrace{100\sqrt{2} \sin(500t + \frac{\pi}{4})}_{\text{AC "1"}}$$

DC "0"

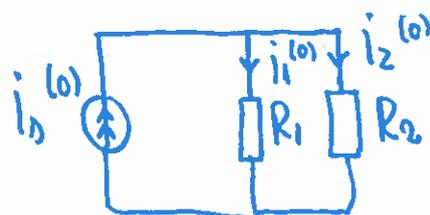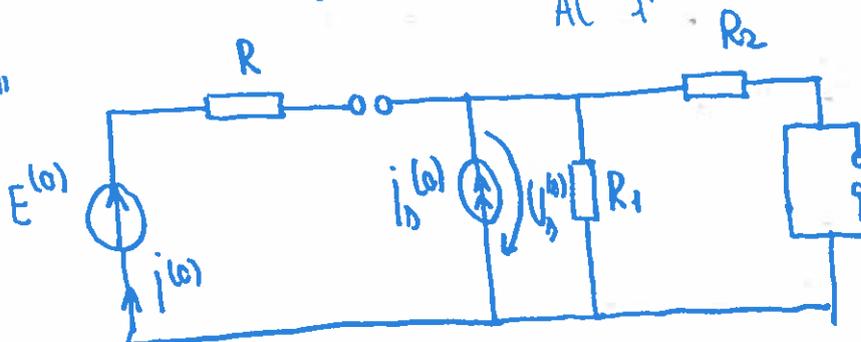


$$i^{(0)} = 0$$

$$i_1^{(0)} = i_2^{(0)} = \frac{i_3^{(0)}}{2} = 1 \text{ A}$$

$$U_0^{(0)} = R_1 i_1^{(0)} = 10 \text{ V}$$

AC "1" ($\omega = 500$)

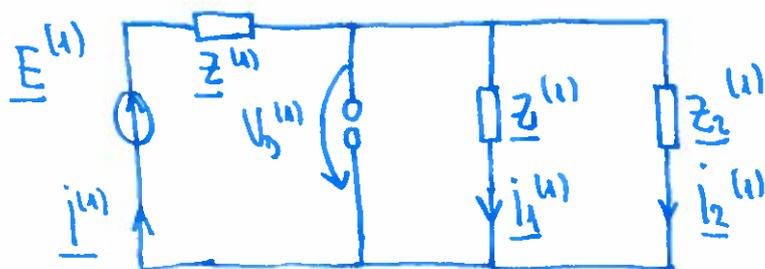

$$\underline{E}^{(\omega)} = 100 e^{j\frac{\pi}{4}} = \frac{100\sqrt{2}}{2} (1+j) = 50\sqrt{2} (1+j)$$

$$\underline{Z}^{(\omega)} = R + j(\omega L - \frac{1}{\omega C}) = 10 + j(4-4) = 10$$

$$\underline{Z}_1^{(\omega)} = R_1 = 10$$

$$\underline{Z}_2^{(\omega)} = R_2 + \frac{\underline{Z}_L \cdot \underline{Z}_C}{\underline{Z}_L + \underline{Z}_C} = 10 + \frac{\frac{L_2}{C_2}}{j(\omega L_2 - \frac{1}{\omega C_2})} = 10 + \frac{1}{j(25-25)}$$

parallel resonant

$$\underline{i}_2^{(\omega)} = 0 \quad (\underline{Z}_2 \rightarrow \infty)$$

$$\underline{i}_1^{(\omega)} = \underline{i}^{(\omega)} = \frac{\underline{E}^{(\omega)}}{\underline{Z}^{(\omega)} + \underline{Z}_1^{(\omega)}} = \frac{50\sqrt{2} (1+j)}{20} = 5 e^{j\frac{\pi}{4}}$$

$$\underline{U}_0^{(\omega)} = \underline{Z}_1^{(\omega)} \cdot \underline{i}_1^{(\omega)} = 50 \frac{\sqrt{2}}{2} (1+j) = 50 e^{j\frac{\pi}{4}}$$

$$i(t) = i_1(t)^{(\omega)} = 5\sqrt{2} \sin(500t + \frac{\pi}{4})$$

$$u(t)^{(\omega)} = 50\sqrt{2} \sin(500t + \frac{\pi}{4})$$

$$i(t) = i^{(0)} + i(t)^{(1)} = 0 + 5\sqrt{2} \sin(500t + \pi/2)$$

$$i_1(t) = i_1^{(0)} + i_1(t)^{(1)} = 1 + 5\sqrt{2} \sin(500t + \pi/4)$$

$$i_2(t) = i_2^{(0)} + i_2(t)^{(1)} = 1 + 0$$

$$u_3(t) = u_3^{(0)} + u_3(t)^{(1)} = 10 + 50\sqrt{2} \sin(500t + \pi/4)$$