

- 14: empty pages:
- 15: 20.12.2016

time varying state of el. circuits (i.e. of el. circuits under time varying cond)



16: Operational calculus of linear dynamic circuits (La Place method)

13: Non sinusoidal

12: Compact

II the direct solution ~~for~~ ^{with} of linear dynamic circ.


Transient State

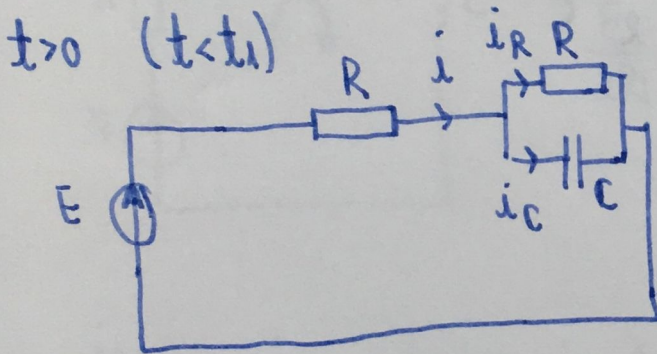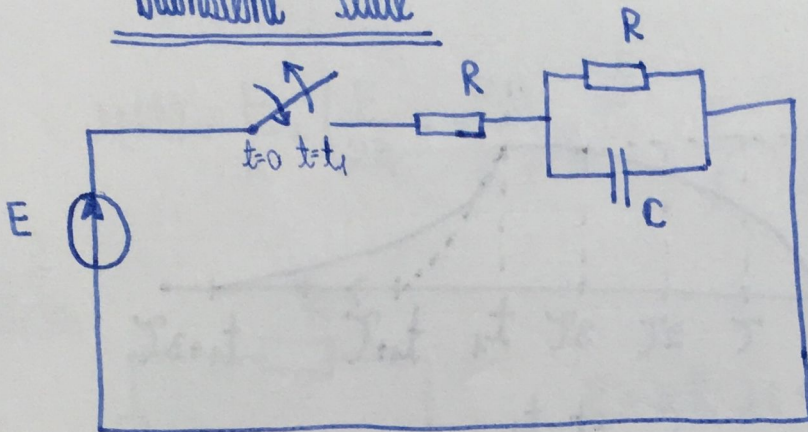

$$\begin{cases} i = i_R + i_C \\ E = R \cdot i + u_C \\ 0 = u_R - u_C \end{cases}$$

$$u_C(t) = u_{C\infty} + (u_{C0+} - u_{C\infty}) \cdot e^{-\frac{t-t_0}{\tau}}$$

\parallel
 $u_{C0-} = 0$

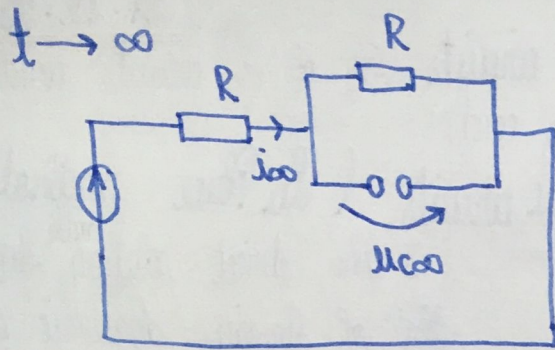


$$i_{\infty} = \frac{E}{2R}$$

$$u_{L\infty} = R \cdot i_{\infty} = R \cdot \frac{E}{2R} = \frac{E}{2}$$


$$\tau = RC$$

↕


$$t_1$$

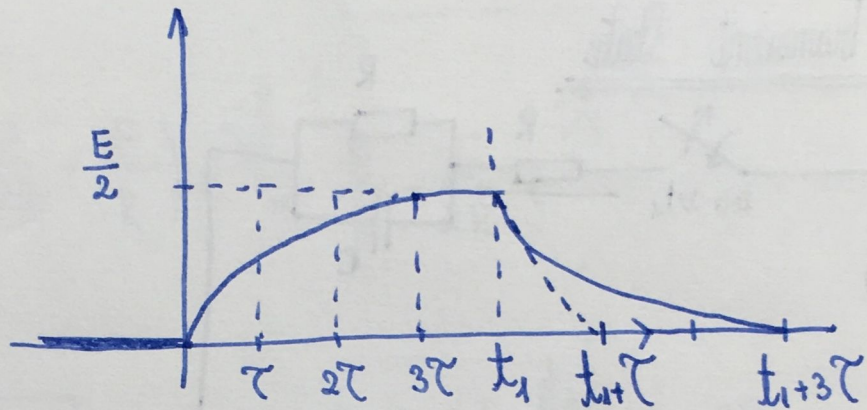
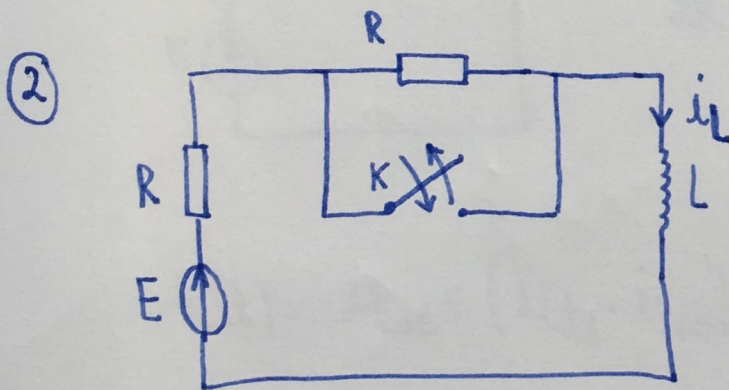
$$\text{II } u_L(t) = u_{L\infty} + (u_{L(t_1+)} - u_{L\infty}) e^{-\frac{t-t_1}{\tau}}$$



$t > 0, t < t_1$

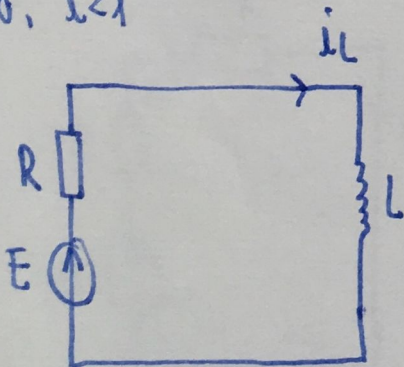



$$E = R \cdot i_L + L \frac{di_L}{dt} \quad | : R$$

$$\frac{E}{R} = i_L + \left(\frac{L}{R}\right) \frac{di_L}{dt}$$

τ


$$i_L(t) = i_{L\infty} + (i_{L(t_1+)} - i_{L\infty}) \cdot e^{-\frac{t-t_1}{\tau}}$$

$t > 0, t \rightarrow \infty$

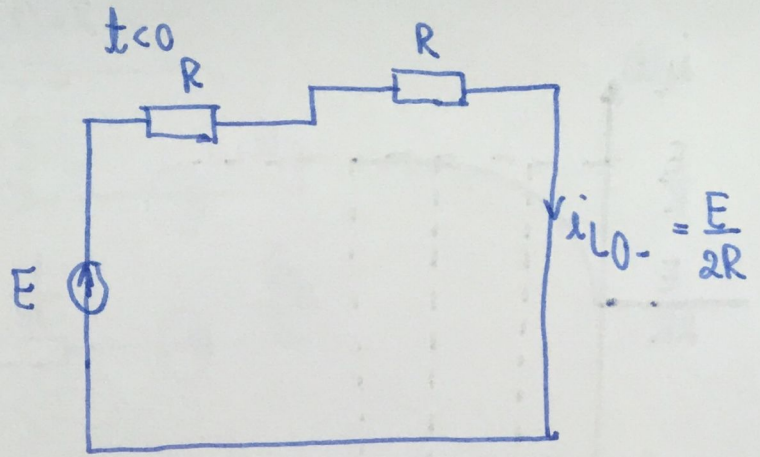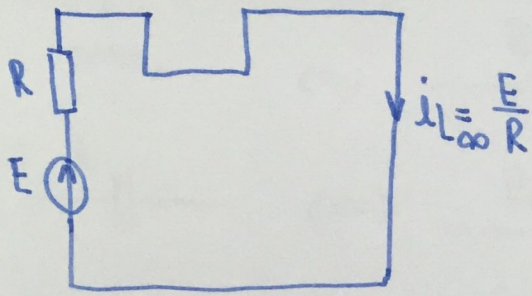

$$i_L(t) = \frac{E}{R} + \left(\frac{E}{2R} - \frac{E}{R} \right) e^{-\frac{t}{\tau}} = \frac{E}{R} - \frac{E}{2R} e^{-\frac{t}{\tau}}$$

$t > t_1$

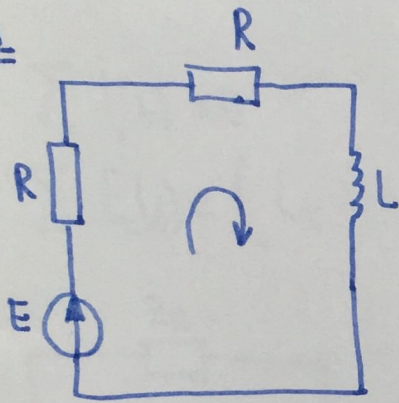


$$E = 2R \cdot i_L + L \frac{di_L}{dt} \quad | : 2R$$

$$\frac{E}{2R} = i_L + \left(\frac{L}{2R} \right) \frac{di_L}{dt} \rightarrow \tau_1$$

$$i_L(t) = i_{L\infty} + (i_{L t_1} - i_{L\infty}) e^{-\frac{t-t_1}{\tau_1}}$$

$t > t_1, t \rightarrow \infty$

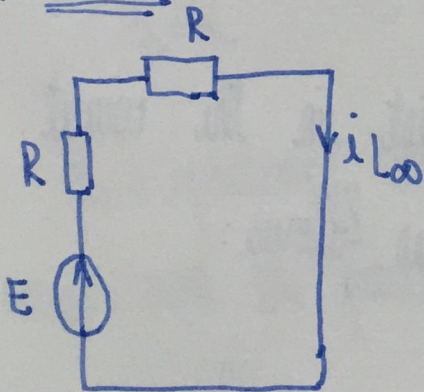

$$i_{L\infty} = \frac{E}{2R}$$


$t < t_1$

$$i_{L t_1+} = i_{L t_1-}$$

a). $t_1 < 3\tau$: $i_{L t_1-} = \frac{E}{R} - \frac{E}{2R} e^{-\frac{t_1}{\tau}}$


b). $t_1 > 3\tau$
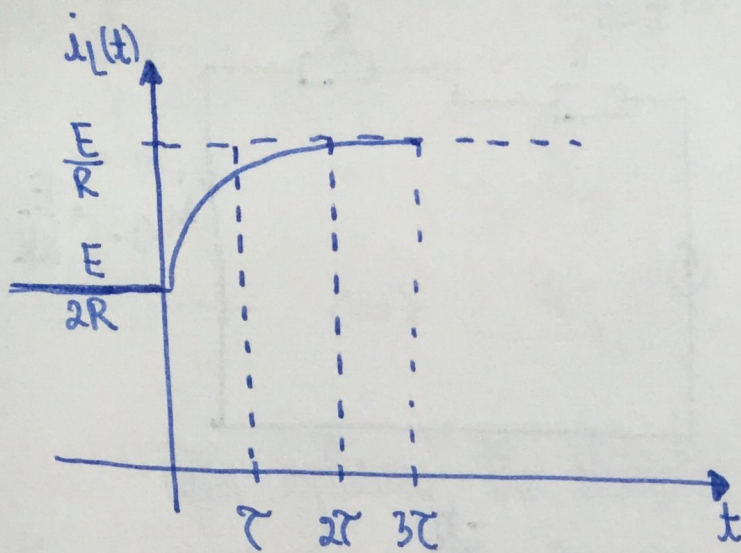
$$i_{L t_1-} = \frac{E}{R} \quad (i_{L\infty}!)$$



$$i_L(t) = \frac{E}{2R} \left(\left\langle \begin{array}{l} \frac{E}{R} - \frac{E}{2R} e^{-\frac{t}{\tau}} \\ \frac{E}{R} \end{array} \right\rangle - \frac{E}{2R} \right) e^{-\frac{t-t_1}{\tau_1}}$$

Laplace method

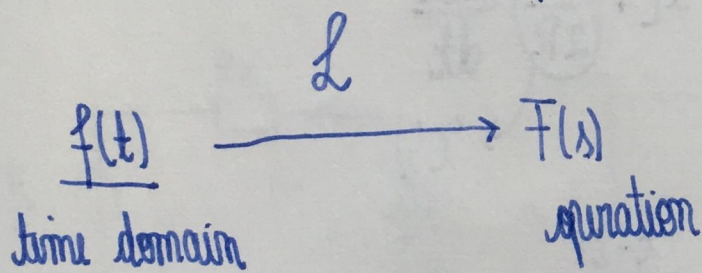


It is generally applied for 2nd order circuits under transient state (the presence of 2 diff. reactive elements in the circuit).

Both inductor and capacitor exist in the circuit.

The circuit will be transformed as follows:


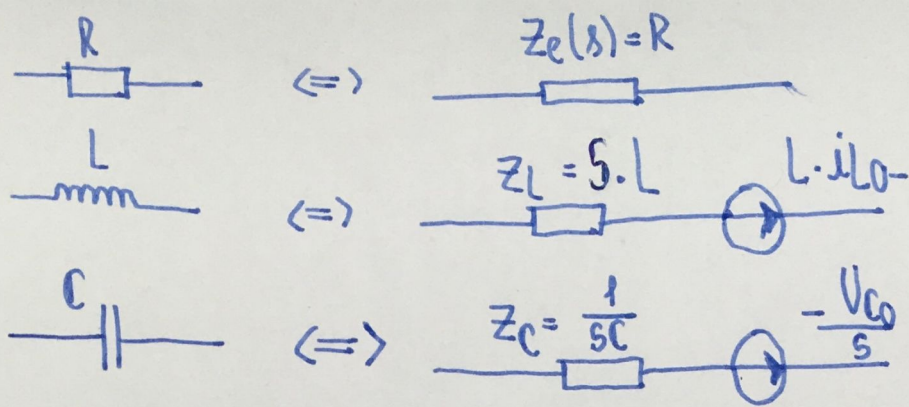
$$E \oplus \Leftrightarrow \oplus \frac{E}{s}, \quad s = \text{Laplace variable}$$



After replacing the elements of the initial circuit by the correspondent operational comp, the equations become linear.

$$i(t) \longrightarrow i(s)$$
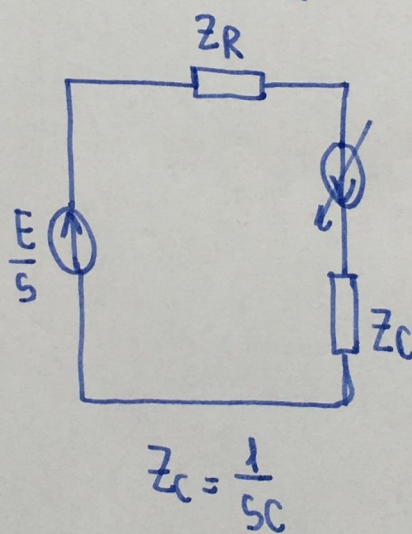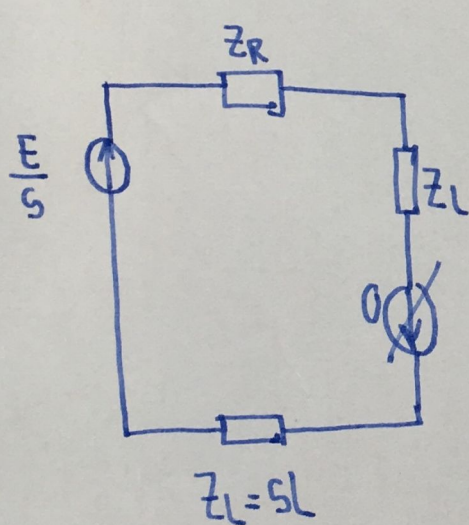
$$\begin{cases} \sum i_k(s) = 0 \\ \sum E_k(s) \pm (L_k i_{L0-k} + \frac{U_{C0-k}}{s}) = \sum_R Z_k(s) \cdot i_k(s) \end{cases}$$



The operational impedances follow the same formula for the series and the parallel connections as the resistors