

Laplace MethodLaplace transforms for the main time $f(t)$

| $f(t)$ | $F(s)$ |
|--|--|
| c | $\frac{c}{s}$ |
| t | $\frac{1}{s^2}$ |
| $e^{\pm \alpha t}$ | $\frac{1}{s \pm \alpha}$ |
| $t \cdot e^{\pm \alpha t}$ | $\frac{1}{(s \pm \alpha)^2}$ |
| $\frac{1}{\alpha} (1 - e^{-\alpha t})$ | $\frac{1}{s} \cdot \frac{1}{s + \alpha}$ |
| $\sin \alpha$ | $\frac{\alpha}{s^2 + \alpha^2}$ |
| $\cos \alpha$ | $\frac{s}{s^2 + \alpha^2}$ |
| $\text{sh } \alpha t$ | $\frac{\alpha}{s^2 - \alpha^2}$ |
| $\text{ch } \alpha t$ | $\frac{s}{s^2 - \alpha^2}$ |
| $t \sin t$ | $\frac{2\alpha s}{(s^2 + \alpha^2)^2}$ |
| $t \cos t$ | $\frac{s^2 - \alpha^2}{(s^2 + \alpha^2)^2}$ |
| $e^{-\beta t} \sin \alpha t$ | $\frac{\alpha}{(s + \beta)^2 + \alpha^2}$ |
| $e^{-\beta t} \cos \alpha t$ | $\frac{s + \beta}{(s + \beta)^2 + \alpha^2}$ |

2nd Method \rightarrow Mellin Fourier

Heaviside $\leftarrow \begin{matrix} 1 \\ 2 \\ \text{gen} \end{matrix}$



Heaviside 1

$$F(s) = \frac{M(s)}{N(s)} \Rightarrow f(t) = \sum_{k=1}^m \frac{M(s_k)}{N'(s_k)} \cdot e^{s_k \cdot t}$$

$N(s_k) = 0$
 \rightarrow simple first order roots

Heaviside 2
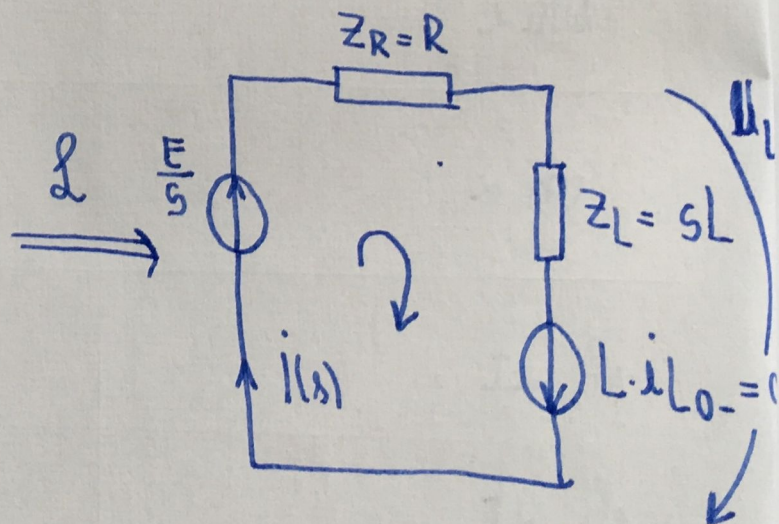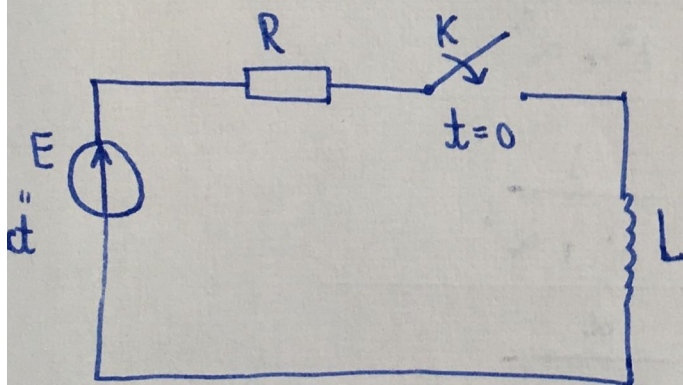
$$F(s) = \frac{M(s)}{s \cdot N(s)} \Rightarrow f(t) = \frac{M(0)}{N(0)} + \sum_k \frac{M(s_k)}{s_k \cdot N'(s_k)} \cdot e^{s_k \cdot t}$$



$$Z_{tot} = Z_R + Z_L = R + sL$$

$$\frac{E}{s} = Z_{tot} \cdot i(s)$$

$$i(s) = \frac{E}{s \cdot (R + sL)}$$

$$i(t) = \frac{E}{R}$$

$$N=0 \Rightarrow R+sL=0$$

$$N'=L$$

$$s_1 = \frac{-R}{L}$$




$$i(t) = \frac{E}{R} + \frac{E}{-\frac{R}{L} \cdot L} e^{\frac{-R}{L} \cdot t} = \frac{E}{R} - \frac{E}{R} e^{\frac{-R}{L} \cdot t} = \frac{E}{R} (1 - e^{\frac{-R}{L} \cdot t})$$

$$u_L = L \frac{di}{dt}$$

$$U_L(s) = Z_L \cdot i(s) - LiL_0 = sL \cdot \frac{E}{s(R+sL)} = \frac{EL}{sL+R}$$

$$H_1 \Rightarrow u_L(t) = \frac{E \cdot L}{L} \cdot e^{s_1 t} = E \cdot e^{s_1 t} = E \cdot e^{\frac{-R}{L} \cdot t}$$
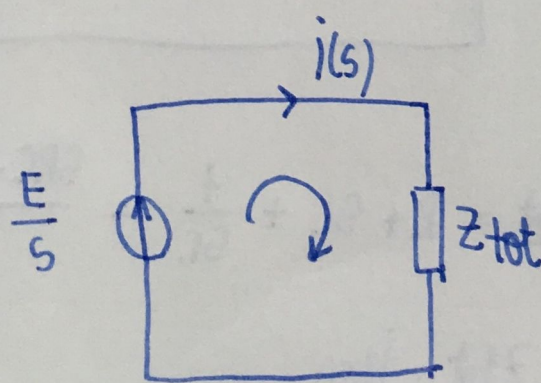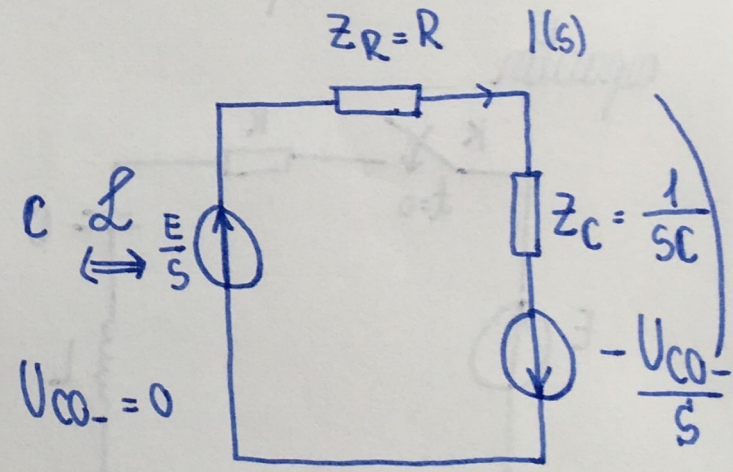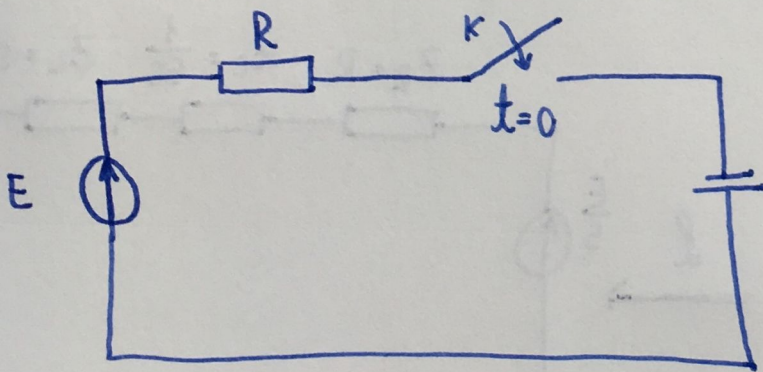
$$N=0 \Rightarrow R+sL=0 \Rightarrow s_1 = \frac{-R}{L}$$



$$Z_{tot} = Z_R + Z_C = R + \frac{1}{sC}$$

$$= \frac{sRC+1}{sC}$$

$$\frac{E}{s} = Z_{tot} \cdot i(s) \Rightarrow i(s) = \frac{E}{s \cdot \frac{sRC+1}{sC}} = \frac{EC}{sRC+1}$$

$$i(t) = \frac{E \cdot C}{RC} \cdot e^{s_1 t} =$$

$$\frac{E}{R} \cdot e^{-\frac{1}{RC} \cdot t}$$

$$N' = RC$$

$$sRC + 1 = 0 \Rightarrow s_1 = -\frac{1}{RC}$$


$$U_C(s) = Z_C \cdot i(s) + \frac{U_{C0-}}{s} = Z_C \cdot i(s) = \frac{1}{sC} \cdot \frac{EC}{sRC+1} = \frac{E}{s(sRC+1)} \quad (H_1)$$

$$= \frac{E}{s(sRC+1)}$$

$$\xrightarrow{H_2} u_C(t) = \frac{M(s)}{N(s)} + \frac{M(s_1)}{s_1 \cdot N'(s_1)} e^{s_1 t} = \frac{E}{1} + \frac{E}{-\frac{1}{RC} \cdot RC} e^{-\frac{1}{RC} \cdot t}$$

$$= E - E e^{-\frac{1}{RC} t} = E \left(1 - e^{-\frac{1}{RC} t} \right)$$

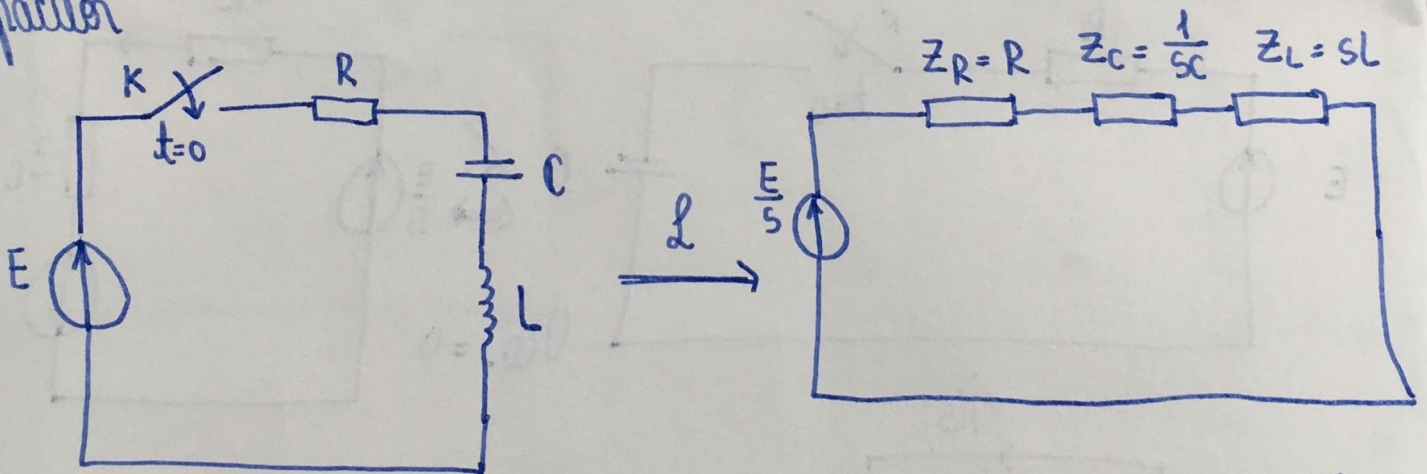Homework: express the current & voltage on the inductor and capacitor



$$R = 30 \Omega$$

$$L = 0.5 \text{ H}$$

$$C = 800 \mu\text{F}$$

$$E = 10 \text{ V}$$

$$U_{C0-} = 0$$

$$U_{L0-} = 0$$

$$Z_{\text{tot}} = R + sL + \frac{1}{sC} = \frac{sRC + s^2LC + 1}{sC}$$

$$\frac{E}{s} = Z_{\text{tot}} \cdot i(s)$$

$$i(s) = \frac{E}{s \cdot \frac{s^2LC + sRC + 1}{sC}} = \frac{EC}{s^2LC + sRC + 1}$$

$$s^2LC + sRC + 1 = 0$$

$$s_1 = \frac{-RC + \sqrt{R^2C^2 - 4LC}}{2LC}$$

$$s_2 = \frac{-RC - \sqrt{R^2C^2 - 4LC}}{2LC}$$

$$\Delta = 30^2 \cdot 64 \cdot 10^4 \cdot 10^{-12} - 4 \cdot \frac{1}{2} \cdot 8 \cdot 10^{-4} = 5,76 \cdot 10^{-4} - 16 \cdot 10^{-4}$$

(H₁)

$$i(t) = \frac{M(s_1)}{N'(s_1)} e^{s_1 t} + \frac{M(s_2)}{N'(s_2)} \cdot e^{s_2 t}$$