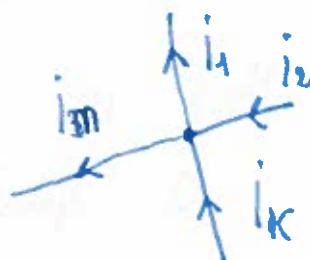


Kirchoff Theorems ①

T1 reference to the currents concurring in one mode of a circuit and it says that the algebraical sum of all the currents concurring in one mode of an electric circuit equals to 0.

$$\sum_{k=1}^m i_k = 0$$



In the algebraical sum, we take with "+" the currents that exit the mode, with "-" currents that enter the mode.


N modes \rightarrow we use K_1 ($N-1$) times

e.g. $i_1 - i_2 - i_k + i_m$

This law is a consequence of the electric charge conservation applied to a closed surface Σ , where the positive direction is considered to be, for the normal unit vector on the respective surface, the outward one.

K₂) \sum of the voltage drops on all the branches of a loop with an electric circuit is 0. $\sum U_K = 0$

$$U_K = R_K \cdot i_K - E_K$$

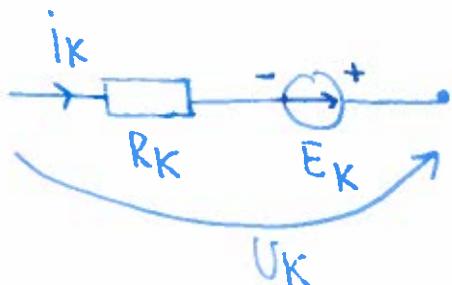

$$\sum R_K i_K = \sum E_K$$

In case that, there are also current sources on the branches of a loop, K₂ equation will contain also the voltage drop on the current source.



K₂ is a consequence of the law of electric conduction, and it can also be consider a consequence of Faraday's law referring to the electromotive force along a closed path under steady-state conditions

The Theory of Power Conservation ⑧ (P. Balance)

It says that the total electric power generated by all voltage, respectively current sources of the circuit, is equal to the total electric power used by the passive elements (resistors).


$P_{gen} = P_{out}$ (received)
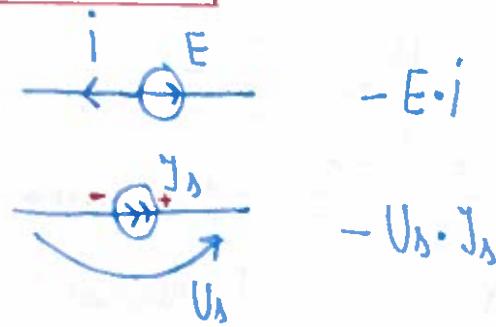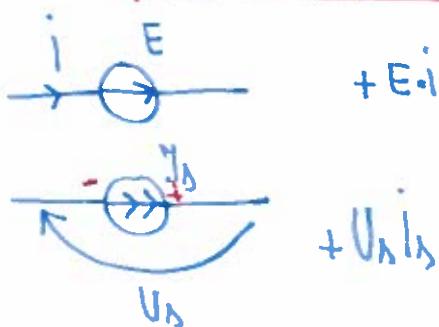
$$P_{gen} = \sum_{K=1} (E_K i_K + U_{sK} i_{sK})$$







The graph of a circuit

Graphs
→ currents
→ voltages
→ oriented

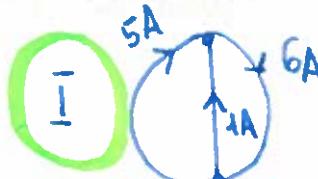

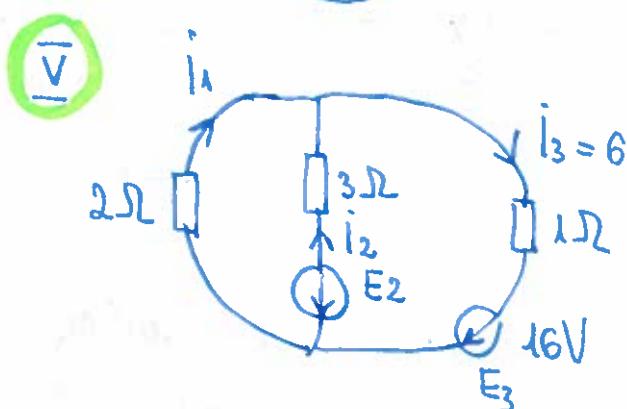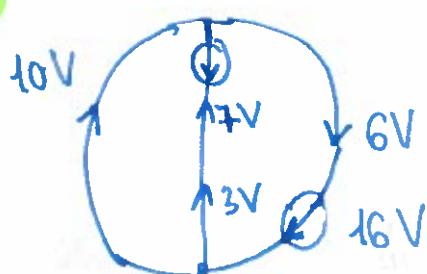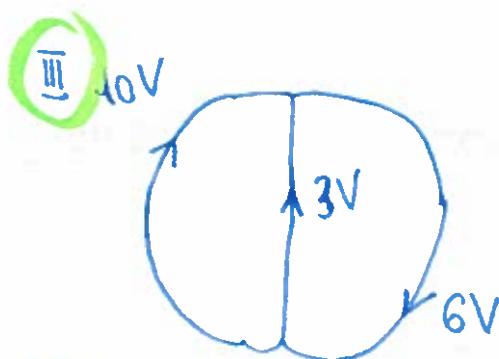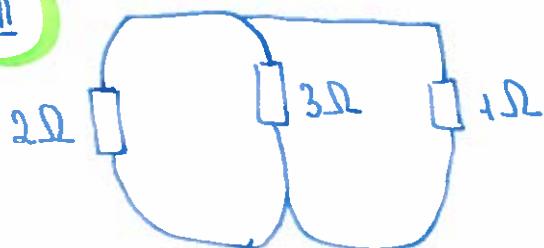A graph is a simplified drawing of a circuit



$R(\Omega)$	$i(A)$	$E(V)$
$R_1 = 2$	$i_1 = 5A$	
$R_2 = 3$	$i_2 = 1A$	$E_2 = 7$
$R_3 = 1$	$i_3 = 6A$	$E_3 = 16$

$$P_{gen} = -E_2 i_2 + E_3 i_3 = 96 - 7 = 89 W$$

$$\begin{aligned} P_{received} &= R_1 i_1^2 + R_2 i_2^2 + R_3 i_3^2 \\ &= 50 + 3 + 36 = 89 W \end{aligned}$$

Homework min 3 Nodes, 5 branches

www.eth.unibw.de/~somad

$$\sum R_K \cdot i_K - U_{bK} = \sum E_K \cdot i_K$$

$$\sum R_K \cdot i_K^2 = \sum E_K \cdot i_K + U_{bK} \cdot i_{bK}$$

Precurred

Pgenerated

$$P = U \cdot i$$

The total power (exchanged power) at the level of a closed ideal circuit is 0

$$P = P_{gen} - P_{prec} = 0$$

The theorem of superposition

Passive







"0" V



--oo--

open

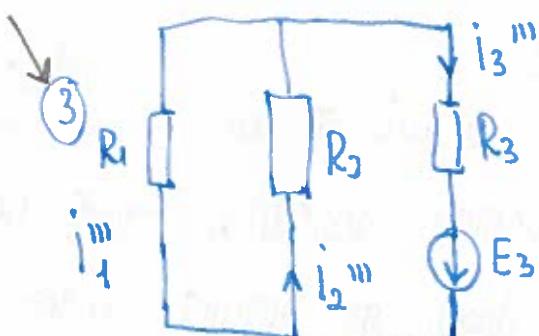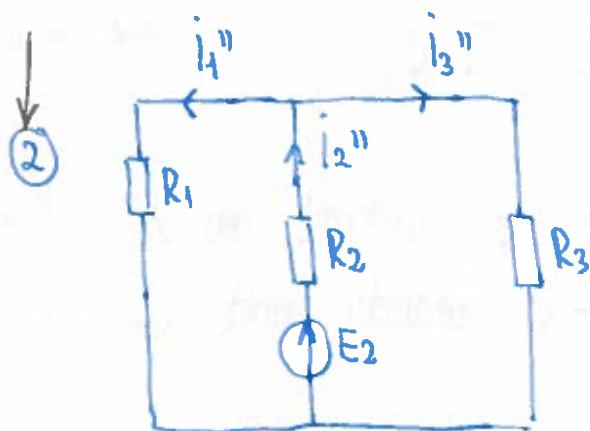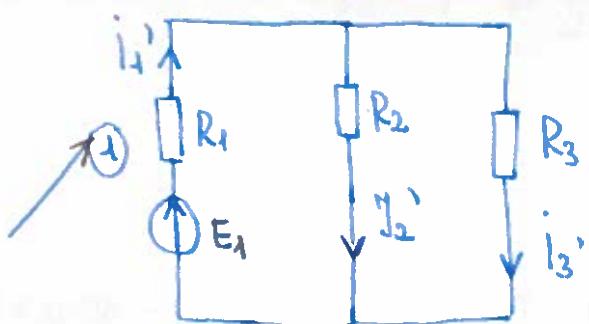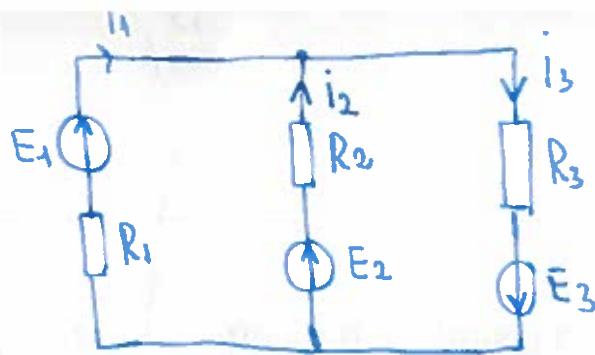It says that : the solution for an electric ideal circuit can be obtained as a superposition as an algebraical sum (linear combination) of the solution obtained in the branches of the circuit if we passivize 1 by 1 the sources, with the rest of them remaining active



$$\left\{ \begin{array}{l} i_1 = i_1' - i_1'' + i_1''' \\ i_2 = -i_2' + i_2'' - i_2''' \\ i_3 = i_3' + i_3'' - i_3''' \end{array} \right.$$

$$i_1' = \frac{E_1}{R_1 + R_{23}}$$

$$i_2' = \frac{i_1 R_3}{R_2 + R_{23}}$$

$$i_3' = \frac{i_1 R_2}{R_2 + R_3}$$

$$i_1'' =$$

$$i_2'' = \frac{E_2}{R_2 + R_{13}}$$

$$i_3'' =$$

$$i_1''' =$$

$$i_2''' =$$

$$i_3''' = \frac{E_3}{R_3 + R_{12}}$$

Kirchoff Method

$$(N-1) \text{ eq. } K_1: \sum_{k=1}^m i_k = 0$$

Euler relation \rightarrow the fundamental number of loops $L = B - N + 1 \rightarrow K \text{ II } \sum V_k = 0$


$$\left. \begin{array}{l} (N-1) + (B-N) \\ = B \text{ branches} \end{array} \right\}$$

in case that:

The circuit contains ^{contain} a number of current sources, then the unknown quantities will be $B-X$ currents and $x = V_{sh}$ (voltage drops on current sources)

The steps for solving such a system of equation are:

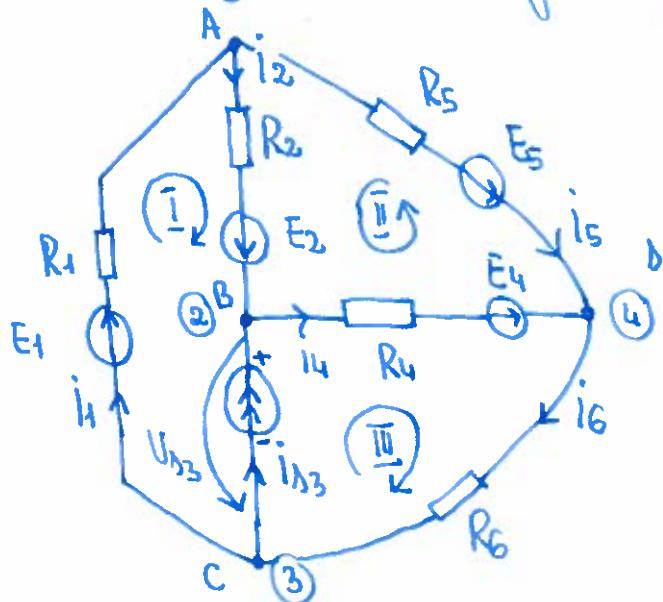- 1). We eliminate some currents from K_1 eq.
- 2) We replace them into the K_2 eq., so as to remain with a system of $B-N+1$ equations
- 3). After replacing numerically the values of the resistances and current sources, we solve the system by using either the reduction/substitution method



$R(\Omega)$	$i(A)$	$E(V)$
$R_1 = 4$	$i_1 = 1$	$E_1 = 5$
$R_2 = 1$	$i_2 = 2$	$E_2 = 5$
R_3	$i_{B3} = 3$	$V_{B3} = 4$
$R_4 = 2$	$i_4 = 5$	$E_4 = 22$
$R_5 = 5$	$i_5 = -1$	$E_5 = 10$
$R_6 = 4$	$i_6 = 4$	

$$\left\{ \begin{array}{l} N=4 \\ B=6 \\ N-1=3 \Rightarrow \text{eq KI} \end{array} \right.$$

$$L=B-N+1 = 6-4+1 = 3 \text{ eq KII}$$

$$\left\{ \begin{array}{l} i_2 + i_5 - i_1 = 0 \\ i_4 - i_{53} - i_2 = 0 \\ i_4 + i_{53} - i_6 = 0 \end{array} \right.$$

$$R_1 i_1 + R_2 i_2 + U_{B3} = E_1 + E_2$$

$$R_2 i_2 + R_4 i_4 - i_5 R_5 = E_2 + E_4 - E_5$$

$$R_4 i_4 - U_{B3} = E_4 + R_6 i_6$$

$$\left\{ \begin{array}{l} 4(i_2 + i_5) + i_2 + U_{B3} = 10 \\ i_2 + 2(i_2 + 3) - 5i_5 = 17 \\ 2(i_2 + 3) + 4(i_2 + i_5 + 3) - U_{B3} = 22 \end{array} \right. \Rightarrow$$

$$\left\{ \begin{array}{l} 5i_2 + 4i_5 + U_{B3} = 10 \\ 3i_2 - 5i_5 = 11 \\ 6i_2 + 4i_5 - U_{B3} = 4 \end{array} \right.$$

$$\left\{ \begin{array}{l} 11i_2 + 8i_5 = 11 \\ 3i_2 - 5i_5 = 11 \end{array} \right.$$

$$79i_5 = -79 \Rightarrow i_5 = -1 \text{ A}$$

$$3i_2 + 5 = 11 \Rightarrow i_2 = 2 \text{ A}$$

$$U_{B3} = 10 - 10 + 4 = 4 \text{ V}$$

$$i_1 = 2 - 1 = 1 \text{ A}$$

$$i_4 = 3 + 2 = 5 \text{ A}$$

$$i_6 = 2 - 1 + 3 = 4 \text{ A}$$

$$P_{\text{gen}} = P_{\text{mechan}}$$

$$\begin{aligned} P_{\text{gen}} &= E_1 i_1 + E_2 i_2 + U_{B3} \cdot i_{B3} + E_4 i_4 + E_5 i_5 \\ &= 5 + 10 + 12 + 110 - 10 = 127 \text{ W} \end{aligned}$$

$$\begin{aligned} P_{\text{mechan}} &= R_1 i_1^2 + R_2 i_2^2 + R_4 i_4^2 + R_5 i_5^2 + R_6 i_6^2 = 4 + 4 + 50 + 5 + 64 \\ &= 127 \text{ W} \end{aligned}$$

$$U_1 = U_{31} = U_{CA} = R_1 i_1 - E_1 = 4 - 5 = -1 \text{ V}$$

$$U_2 = U_{AB} = R_2 i_2 - E_2 ; \quad U_{BA} ; \quad U_2 = 2 - 5 = -3 \text{ V}$$

$$U_3 = U_{BC} = U_{S3} = 4 \text{ V}$$

$$U_4 = R_4 i_4 - E_4 = 10 - 22 = -12 \text{ V}$$

$$U_5 = i_5 R_5 - E_5 = -5 - 10 = -15 \text{ V}$$

$$U_6 = i_6 R_6 = 16 \text{ V}$$