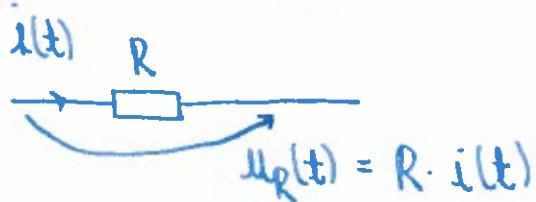


Alternating Currents (AC) Circuits

$$f(t) \quad (i(t), v(t), i_5(t), u_5(t))$$

$$f(t) = \mp\sqrt{2} \sin(\omega t + \varphi)$$

The AC circuits contain sinusoidal time variable sources and as receptors they contain resistors and reactive elements (capacitors & inductors)



$$u_R(t) = R \cdot i(t)$$

The equation of the resistor is a linear one:

$$C \quad \begin{array}{c} + \\ || \\ - \end{array}$$



$i(t)$

$$u_C(t) = \frac{1}{C} \int i(t) dt$$

$$i = \frac{du}{dt} \quad C = \frac{q}{u_C} \Rightarrow q = C \cdot u_C$$

$$i = C \cdot \frac{du_C}{dt}$$
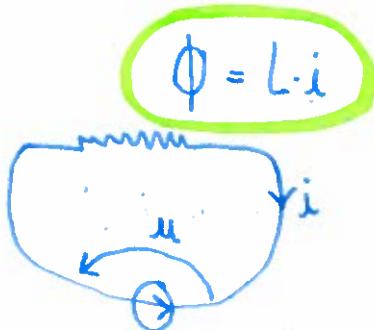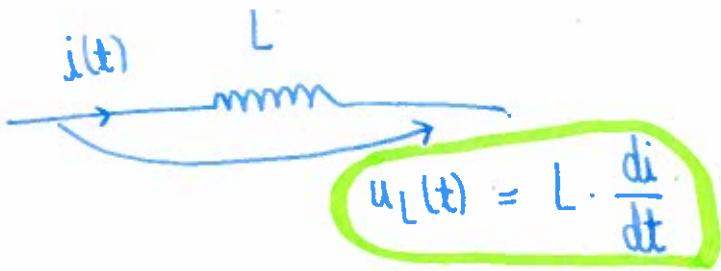
$$\int i dt = C \int \frac{du_C}{dt} dt \Rightarrow \frac{1}{C} \int i dt = u_C$$



$$e_r = -\frac{d\phi}{dt} \quad [\phi] = \text{Wb}$$

$$u_L = -e_r = \frac{d\phi}{dt} = L \cdot \frac{di}{dt}$$

$f(t) = \underbrace{\mp \sqrt{2}}_{\text{max.}} \sin(\omega t + \varphi)$

$$\omega = 2\pi f$$

$\varphi$  = phase

$\mp$  = instantaneous value

$$\left\{ \begin{array}{l} \sum_{k=1}^n i_k h_k = 0 \\ \sum_{k=1}^n [(u_{r_k}(t) + u_{L_k} + u_{C_k}) + U_{S_k}] = \sum e_k(t) \end{array} \right.$$

Review: complex numbers! + trig. circle

$$a + bj$$







$$r(\cos \varphi + j \sin \varphi)$$

$$r = \sqrt{a^2 + b^2}$$

$$\varphi = \arctan \frac{b}{a}$$

$$\underline{F} = F \cdot \exp(j\phi)$$
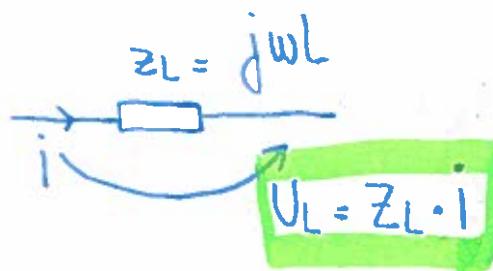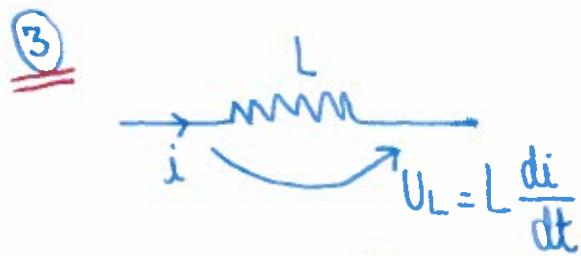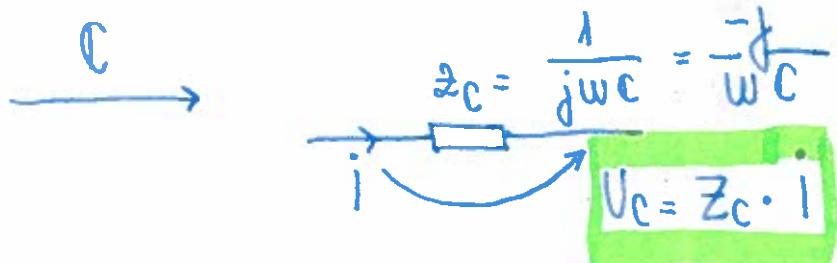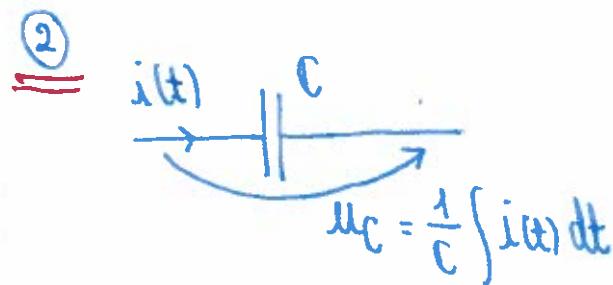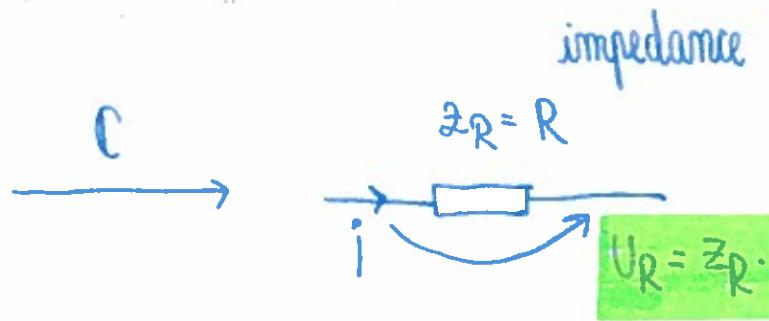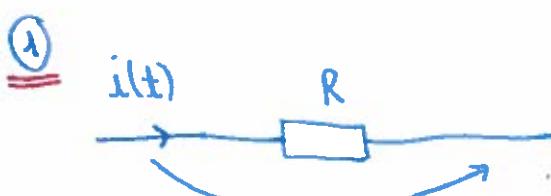
$$e^{j\phi} = (\cos \phi + j \sin \phi)$$




$$i = a + bj = \sqrt{a^2 + b^2} \left( \cos \phi_i + j \sin \phi_i \right)$$

$$\phi_i = \arctg \frac{b}{a}$$

$$i(t) = I\sqrt{2} \sin(\omega t + \phi_i)$$


Example:

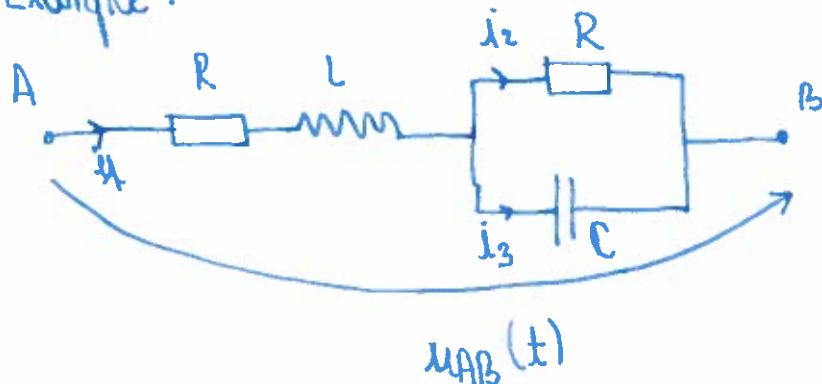

$$U_{AB}(t) = 60\sqrt{2} \sin(500t + \frac{\pi}{2})$$

$$R = 10 \Omega \quad L = 40 \text{ mH}$$

$$C = 0.2 \text{ mF}$$

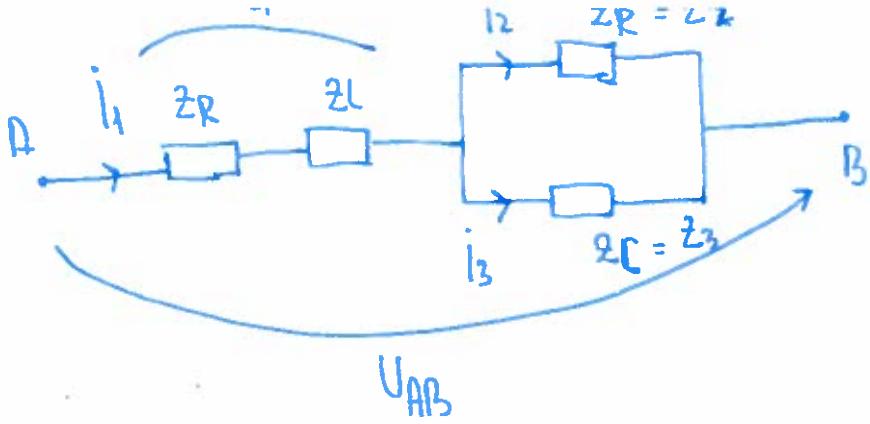

$$U_{AB} = 60$$

$$U_{AB \text{ max}} = 60\sqrt{2}$$

$$\omega = 500$$

$$\varphi = \frac{\pi}{2}$$

$$U_{AB} = U_{AB} \cdot e^{j\varphi} = 60 \left( \cos \frac{\pi}{2} + j \sin \frac{\pi}{2} \right) = 60j$$

$$Z_R = R = 10$$

$$Z_L = j\omega L = j \cdot 500 \cdot 40 \cdot 10^{-3} = 20j$$

$$Z_C = \frac{-j}{\omega C} = -j \cdot \frac{1}{500 \cdot 2 \cdot 10^{-4}} = -10j$$

equiv. transformation:

$$Z_S = \sum z_k$$

$$Z_P = \frac{1}{\sum \frac{1}{z_k}}$$

$$\left\{ Y = \frac{1}{Z} \right. \quad \text{admittance}$$

$$\left\{ \begin{array}{l} \underline{wL = X_L} \text{ } (\Omega) \rightarrow \text{inductive reactance} \\ \underline{X_C = \frac{1}{\omega C}} \text{ } (\Omega) \rightarrow \text{capacitive reactance} \end{array} \right.$$

$$Z_L = j \cdot X_L$$

$$Z_C = -j \cdot X_C$$

## Current divider

$$I_2 = I_1 \frac{Z_3}{Z_2 + Z_3}$$


$$I_3 = I_1 \frac{Z_2}{Z_2 + Z_3}$$

$$Z_{23} = \frac{Z_2 \cdot Z_3}{Z_2 + Z_3} = \frac{Z_R Z_C}{Z_R + Z_C} = \frac{10 \cdot -10j}{10 - 10j} = \frac{-10j}{1-j} =$$

$$Z_{23} = \frac{-10j(1+j)}{2} = -5j(1+j) = 5 - 5j$$

$$Z_1 = Z_R + Z_L = 10 + 20j$$
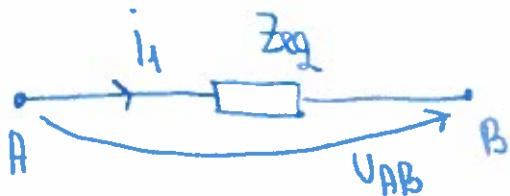
$$Z_{eq} = Z_1 + Z_{23} = 10 + 20j + 5 - 5j = 15 + 15j = 15(1+j)$$



$$i_1 = \frac{V_{AB}}{Z_{eq}} = \frac{60}{15(1+j)} = 4j \frac{(1-j)}{2} = 2(1+j)$$

$$i_2 = \frac{2(1+j) \cdot -10j}{10 + 20j} = -2j \frac{(1+j)(1-2j)}{5} = 2A$$

$$i_3 = i_1 \frac{Z_2}{Z_2 + Z_3} = 2j$$

$$i_1 = i_2 + i_3$$

$$i_1 = \sqrt{4+4} \cos \frac{\pi}{4} + j \sin \frac{\pi}{4} = 2\sqrt{2} e^{j\pi/4}$$

$$i_2 = 2e^{j0^\circ}$$

$$i_3 = 2 \left( \cos \frac{\pi}{2} + j \sin \frac{\pi}{2} \right) = 2e^{j\pi/2}$$

$$I_1 = (2\sqrt{2})e^{j\pi/4}$$

$$i_1(t) = 2\sqrt{2} \cdot \sin(500t + \pi/4)$$

$$I_2 = (2)e^{j0}$$

$$i_2(t) = 2\sqrt{2} \sin(500t + 0)$$

$$I_3 = (2)e^{j\pi/2}$$

$$i_3(t) = 2\sqrt{2} \sin(500t + \pi/2)$$