

BE CURST

8.11.2016

$$\underline{Z}_e = R_e + j X_e \quad Z_e = \sqrt{R_e^2 + X_e^2} \quad Y_e = \sqrt{G_e^2 + B_e^2}$$

$$\underline{Y}_e = G_e - j B_e \quad R_e = \operatorname{Re}\{Z\}$$

$$\left\{ \begin{array}{l} G_e = \text{conductance} \\ B_e = \text{susceptance} \end{array} \right. \quad X_e = \operatorname{Im}\{Z\}$$

$$G_e = \operatorname{Re}\{Y\} \quad B_e = -\operatorname{Im}\{Y\}$$

$$Z = \frac{1}{Y} \quad R = \frac{1}{G}$$


Loop Current

$$\left\{ \begin{array}{l} \sum_{j=1}^L \underline{Z}_{hj} \underline{i}'_j = \sum \underline{E}'_h \quad h = \overline{1, L} \quad L = B-N+1 \\ \left\{ \begin{array}{l} \underline{Z}_{11} \underline{i}'_1 + \underline{Z}_{12} \underline{i}'_2 + \dots + \underline{Z}_{1L} \underline{i}'_L = \underline{E}'_1 \\ \underline{Z}_{L1} \underline{i}'_1 + \underline{Z}_{L2} \underline{i}'_2 + \dots + \underline{Z}_{LL} \underline{i}'_L = \underline{E}'_2 \end{array} \right. \end{array} \right.$$

Node Potential Method

$$\left\{ \begin{array}{l} \sum_{j=1}^{N-1} Y_{ij} V_j = I_{DCi} \quad i = \overline{1, N-1} \\ \underline{Y}_{11} V_1 + \underline{Y}_{12} V_2 + \dots + \underline{Y}_{1N-1} V_{N-1} = I_{DC1} \\ \dots \dots \dots \dots \dots \dots \dots \dots \\ \underline{Y}_{N-1,1} V_1 + \underline{Y}_{N-1,2} V_2 + \dots + \underline{Y}_{N-1,N-1} V_{N-1} = I_{DCN-1} \end{array} \right.$$

## Series Connection

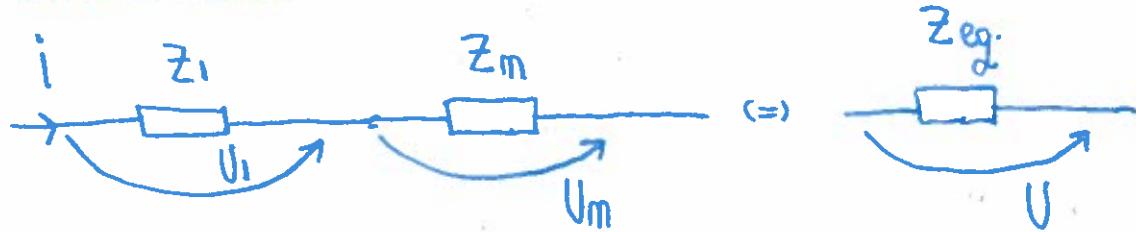


$$Z_{eq} = \sum z_k$$

$$U = U_1 + \dots + U_m = z_1 i + \dots + z_m i = (z_1 + \dots + z_m) \cdot i$$

$$U_k = z_k \cdot i = z_k \cdot \frac{U}{Z_{eq}}$$

## Parallel

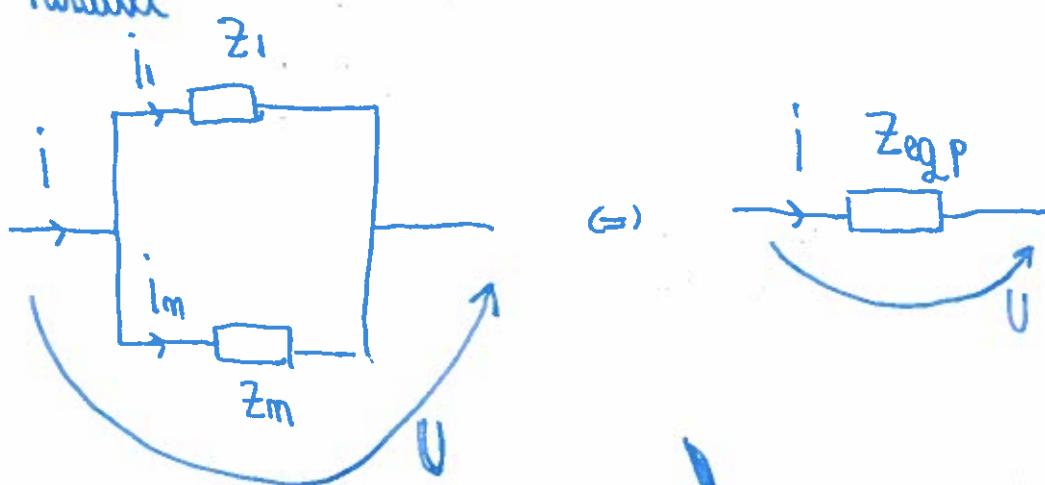

$$i = i_1 + \dots + i_m$$

$$\frac{U}{Z_{eqp}} = \frac{U}{z_1} + \dots + \frac{U}{z_m}$$

$$i_k = \frac{U}{z_k} = \frac{i \cdot Z_{eqp}}{z_k}$$

$$Z_{eqp} = \frac{1}{\sum_k \frac{1}{R_k}} = \frac{1}{\sum_k Y_k}$$

$$\left\{ \begin{array}{l} i_1 = \frac{i Z_2}{Z_1 + Z_2} \\ i_2 = \frac{i \cdot Z_1}{Z_1 + Z_2} \end{array} \right.$$

$$\underline{z}_e = \underline{z} \quad E_e = \underline{E} + \underline{z} \cdot \underline{i}$$

$$i_{de} = i_s + E \cdot Y$$

$$Y = \frac{1}{\underline{z}}$$

$$\underline{z}_e = \sum \underline{z}_k$$


$$E_e = \sum E_k \quad (\text{algebraical})$$

$$\underline{z}_e = \frac{1}{\sum Y_k}$$

$$E_e = \frac{\sum E_k Y_k}{\sum Y_k}$$

algebraical

EX:

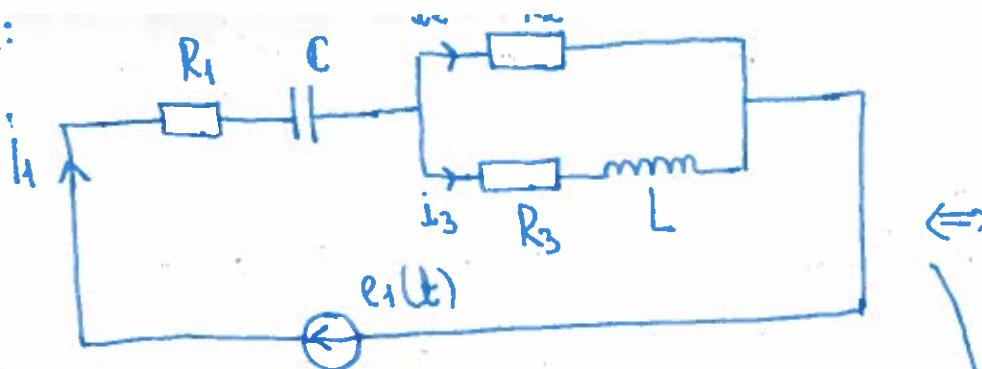

$$e_1(t) = 20\sqrt{2} \sin(100t - \frac{\pi}{3}) \text{ (V)}$$

$$R_1 = R_3 = 5 \Omega \quad R_2 = 10 \Omega$$


$$L = 50\sqrt{3} \text{ mH} \quad C = \frac{2}{\sqrt{3}} \text{ mF}$$

$$f(t) = \mp\sqrt{2} \sin(\omega t + \varphi) \quad \mp = f \cdot e^{j\varphi}$$

$$E_1 = 20$$

$$\omega = 100$$

$$\varphi = -\frac{\pi}{3}$$

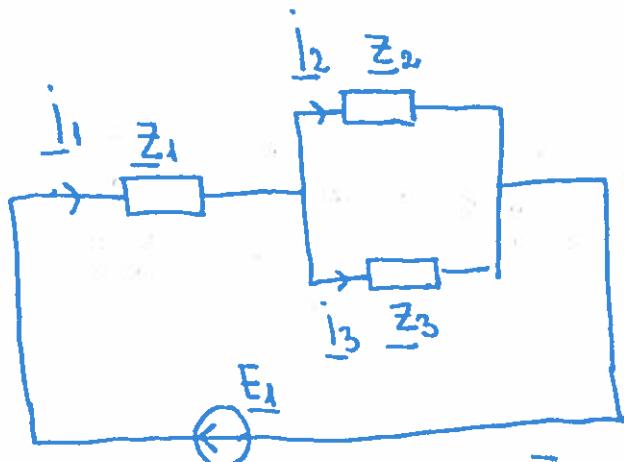

$$\underline{E}_1 = E_1 e^{j\varphi} = 20 e^{j - \frac{\pi}{3}}$$

$$\underline{E}_1 = 20 \underbrace{\cos\left(-\frac{\pi}{3}\right)}_{\frac{1}{2}} + j \underbrace{\sin\left(-\frac{\pi}{3}\right)}_{-\frac{\sqrt{3}}{2}} = 10(1 - \sqrt{3}j)$$

$$\underline{Z}_1 = \underline{Z}_{R_1} + \underline{Z}_C = R_1 + j \cdot \frac{1}{\omega C} = 5 + j \frac{1}{10^2 \cdot \frac{2}{\sqrt{3}} \cdot 10^{-3}} \\ = 5 - 5\sqrt{3}j$$

$$\underline{Z}_2 = \underline{Z}_{R_2} = 10$$

$$\underline{Z}_3 = \underline{Z}_{R_3} + \underline{Z}_L = R_3 + j\omega L = 5 + j \cdot 10^2 \cdot 50\sqrt{3} \cdot 10^{-3} = 5 + 5\sqrt{3}j$$

$$Z_{eq} = Z_1 + Z_{23}$$

$$Z_{23} = \frac{z_2 z_3}{z_2 + z_3} = \frac{10 \cdot 5(1 + \sqrt{3}j)}{5(3 + \sqrt{3}j)}$$

$$= \frac{10(3 + 3\sqrt{3}j) - \sqrt{3}j + 3}{12} = \frac{10(6 + 2\sqrt{3}j)}{12\sqrt{3}} = \frac{5(3 + \sqrt{3}j)}{3}$$

$$Z_{eq} = 5 - 5\sqrt{3}j + \frac{5(3 + \sqrt{3}j)}{3} = \frac{15 - 15\sqrt{3}j + 15 + 5\sqrt{3}j}{3} = \frac{30 - 10\sqrt{3}j}{3}$$

$$i = \frac{E_1}{Z_{eq}} = \frac{10(1 - \sqrt{3}j) \cdot 3}{10(3 - \sqrt{3}j)} = \frac{3(1 - \sqrt{3}j)}{(3 - \sqrt{3}j)} = \frac{3(1 - \sqrt{3}j)(3 + \sqrt{3}j)}{12}$$

$$= \frac{3 + \sqrt{3}j - 3\sqrt{3}j + 3}{4} = \frac{3 - \sqrt{3}j}{2}$$

$$i_1 = \frac{3 - \sqrt{3}j}{2} = \frac{\sqrt{3}}{2} (1 - j) = \sqrt{3} \left( \frac{\sqrt{3}}{2} - \frac{j}{2} \right) = \sqrt{3} \left( \cos \left( -\frac{\pi}{6} \right) + j \sin \left( -\frac{\pi}{6} \right) \right)$$

$$= \sqrt{3} \cdot \cos \left( -\frac{\pi}{6} \right) + j \sin \left( -\frac{\pi}{6} \right)$$

$$\rightarrow i_1(t) = \sqrt{3} \cdot \sqrt{2} \cdot \sin \left( 100t - \frac{\pi}{6} \right) \quad (\text{A})$$

$$i_2 = i \frac{z_3}{z_2 + z_3} = \frac{3 - \sqrt{3}j}{2} \frac{5(1 + \sqrt{3}j)}{5(3 + \sqrt{3}j)} = \frac{(9 - 6\sqrt{3} - 3j)(1 + \sqrt{3})}{2 \cdot 12}$$

$$= \frac{2(3 - \sqrt{3}j)(1 + \sqrt{3}j)}{2 \cdot 12} = \frac{3 + \sqrt{3}j}{6} = \frac{\sqrt{3}}{6} (1 + \sqrt{3}j)$$

$$i_2 = \frac{\sqrt{3}}{3} \left( \frac{\sqrt{3}}{2} + \frac{1}{2}j \right) = \frac{\sqrt{3}}{3} e^{j\frac{\pi}{6}}$$

$$\rightarrow i_2(t) = \frac{\sqrt{3}}{3} \cdot \sqrt{2} \cdot \sin \left( 100t + \frac{\pi}{6} \right)$$

$$i_3 = i_1 - i_2 = \frac{3\sqrt{3}j}{2} = \frac{3+\sqrt{3}j}{6} = \frac{6-4\sqrt{3}j}{6} = \frac{3-2\sqrt{3}j}{3}$$

$$\underline{i}_3 = \frac{3-\sqrt{3}j}{2} - 1 = \frac{1-\sqrt{3}j}{2} = 1 \left( \frac{1}{2} - \frac{\sqrt{3}}{2} j \right) = 1 \cdot e^{j\left(\frac{-\pi}{3}\right)}$$

$$\rightarrow i_3(t) = \sqrt{2} \cdot \sin(100t - \frac{\pi}{3})$$

