
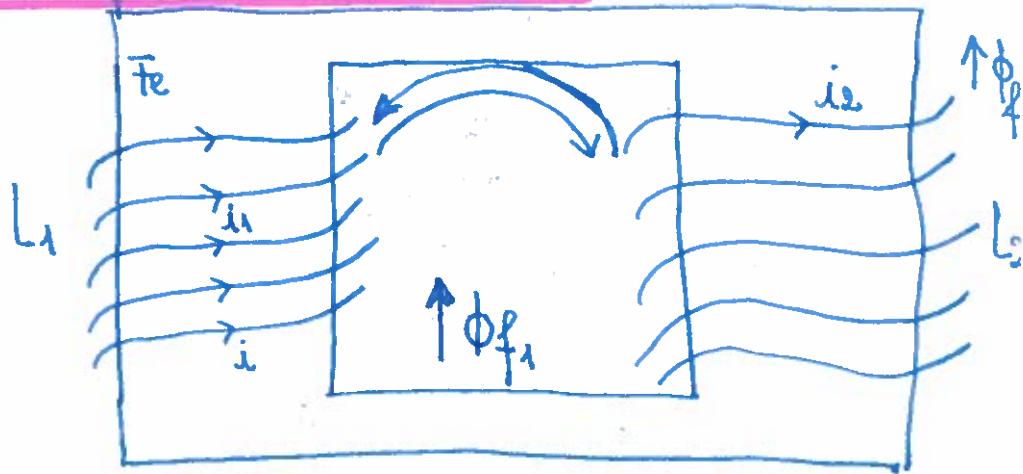


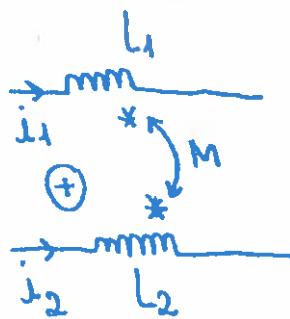AC Circuits with coupled coils (inductors)




$$\mathcal{U}_L = \frac{d\Phi}{dt} = L \frac{di}{dt}$$

$$\mathcal{U}_{L_1} = \frac{L_1 di}{dt} \pm M \frac{di_2}{dt}$$
 (mutual inductance (H))

$$\mathcal{U}_{L_2} = \frac{L_2 di}{dt} \pm M \frac{di_1}{dt}$$

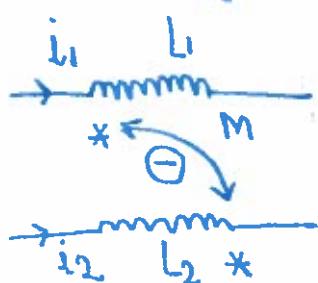
When both currents have the same orientation with respect to such called polarised terminals, then we choose "+".
When they have opposite orientation, we choose "-".



$$\underline{\mathcal{U}}_{L_1} = j\omega L_1 \cdot \underline{i_1} \pm j\omega M \cdot \underline{i_2}$$

$$\underline{\mathcal{U}}_{L_2} = j\omega L_2 \cdot \underline{i_2} \pm j\omega M \cdot \underline{i_1}$$

EX:

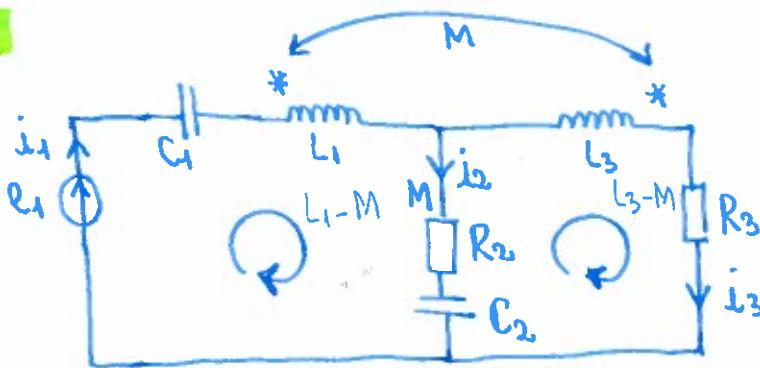

$$e_1(t) = 160 \sin(100t + \pi/4)$$

$$R_2 = 40 \Omega \quad R_3 = 40 \Omega$$

$$L_1 = 0.8 \text{ H} \quad L_3 = 0.6 \text{ H}$$

$$C_2 = \frac{1}{6} \text{ mF} \quad C_1 = 0.1 \text{ mF}$$

$$M = 0.2 \text{ H}$$

$$\left\{ \begin{array}{l} i_1 = i_2 + i_3(t) \\ e_1 = \underbrace{\frac{1}{C_1} \int i_1 dt}_{U_{C_1}} + \underbrace{L_1 \frac{di_1}{dt}}_{U_{L_1}} - M \frac{di_3}{dt} + \underbrace{R_2 i_2}_{U_{R_2}} + \underbrace{\frac{1}{C_2} \int i_2 dt}_{U_{C_2}} \\ 0 = -\underbrace{\frac{1}{C_2} \int i_2 dt}_{U_{C_2}} - \underbrace{R_2 i_2}_{U_{R_2}} + \underbrace{L_3 \frac{di_3}{dt}}_{U_{L_3}} - M \frac{di_1}{dt} + \underbrace{R_3 i_3}_{U_{R_3}} \end{array} \right. \iff$$

$$\left\{ \begin{array}{l} i_3 = i_1 - i_2 \\ I_1 = \frac{1}{C_1} \int i_1 dt + L_1 \frac{di_1}{dt} - M \frac{di_1}{dt} + M \frac{di_2}{dt} + R_2 i_2 + \frac{1}{C_2} \int i_2 dt \\ 0 = -\frac{1}{C_2} \int i_2 dt - R_2 i_2 + \cancel{(L_3)} \frac{di_3}{dt} - \cancel{M} \frac{di_2}{dt} - \cancel{M} \frac{di_3}{dt} + \cancel{(R_3)} i_3 \end{array} \right.$$


$$\begin{array}{ll} I & i_1 \rightarrow (L_1 - M) \quad i_3 \rightarrow (L_3 - M) \\ & i_2 \rightarrow M \quad i_2 \rightarrow -(C_2 + R_2 + M) \end{array}$$

RULE If the polarised terminals are equally distanced from the common mode (if the branches containing a couple coils), then we can cancel the coupling by introducing the inductance " $-M$ " on both branches that are coupled and adding an inductance M to the third neutral branch connected to the same mode.



b). In case that the polarised terminals are differently distanced from the common mode, then we can cancel the coupling by adding " $+M$ " on those branches and adding " $-M$ " on the third neutral branch.

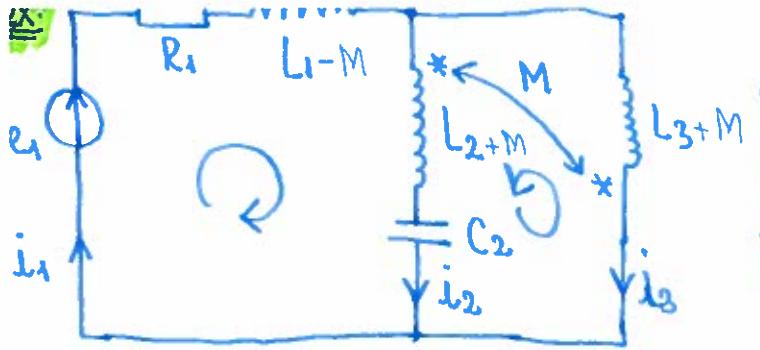In case that, the neutral branch already contains another independent coil, then " $+M$ ", respectively " $-M$ " will be added to the existing one



$$e_1(t) = 240 \sin(100t - \pi/2)$$

$$R_1 = 60 \Omega$$

$$L_2 = 0.4 \text{ H}$$

$$L_3 = 1 \text{ H}$$

$$L_1 = 0.2 \text{ H}$$


$$C_2 = 0.1 \text{ mF}$$

$$M = 0.2 \text{ H}$$

$$L_2' = L_2 + M = 0.6 \text{ H}$$

$$L_3' = L_3 + M = 1.2 \text{ H}$$

$$L_1' = L_1 - M = 0$$

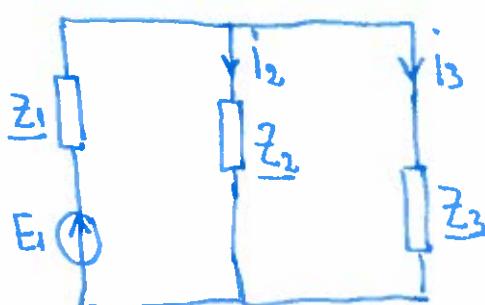

$$E_1 = 240 = X\sqrt{2} \Rightarrow X = 120\sqrt{2}$$

$$\underline{Z}_{eq} = \underline{Z}_1 + \underline{Z}_{23} = 60 + \frac{\underline{Z}_2 \underline{Z}_3}{\underline{Z}_2 + \underline{Z}_3} = 60 + \frac{60 \cdot (-40j) \cdot 120j}{60 + (-40j) + 120j} = 60(1-j)$$

$$I_1 = \frac{E_1}{\underline{Z}_{eq}} = \frac{-120\sqrt{2}j}{60(1-j)} = \frac{-2\sqrt{2}j(1+j)}{2} = \frac{2\sqrt{2}}{2}(1-j)$$

$$\begin{aligned}
 i_1 &= i_2 + i_3 \\
 e_1 &= R_1 i_1 + L_1 \frac{di_1}{dt} + L_2 \frac{di_2}{dt} - M \frac{di_3}{dt} + \frac{1}{C_2} \int i_2 dt \\
 0 &= L_2 \frac{di_2}{dt} - M \frac{di_3}{dt} - (L_3 \frac{di_3}{dt} - M \frac{di_2}{dt}) + \frac{1}{C_2} \int i_2 dt
 \end{aligned}$$

$$\underline{Z}_1 = R_1 + j\omega L_1 = 60$$

$$\underline{Z}_2 = j(\omega L_2' - \frac{1}{\omega C_2}) = j(60 - 100) = -40j$$

$$\underline{Z}_3 = j\omega L_3' = j \cdot 100 \cdot 1.2 = 120j$$

$$E_1 = 120\sqrt{2} e^{j(-\frac{\pi}{2})}$$

$$\begin{aligned}
 &= 120\sqrt{2} \left(\cos\left(-\frac{\pi}{2}\right) + j \sin\left(-\frac{\pi}{2}\right) \right) \\
 &= -120\sqrt{2}j
 \end{aligned}$$

$$60 \cdot \frac{60}{80} = 45$$


$$\underline{I_1} = 2 \left(\frac{\sqrt{2}}{2} - \frac{\sqrt{2}}{2} j \right) = 2 e^{j - \frac{\pi}{4}} \Rightarrow i_1(t) = 2\sqrt{2} \sin(100t - \frac{\pi}{4})$$

$$\underline{I_2} = \underline{i_1} \cdot \frac{\underline{Z_3}}{\underline{Z_3} + \underline{Z_2}} = \sqrt{2}(1-j) \cdot \frac{120j}{80j} = \frac{3\sqrt{2}}{2}(1-j) = 3e^{j - \frac{\pi}{4}}$$

$$\underline{I_3} = \underline{i_1} \frac{\underline{Z_2}}{\underline{Z_2} + \underline{Z_3}} = \sqrt{2}(1-j) \cdot \frac{-40j}{80j} = \frac{\sqrt{2}}{2}(-1+j) = 1 \cdot e^{j \frac{3\pi}{4}}$$

$$i_2(t) = 3\sqrt{2} \sin(100t - \frac{\pi}{4})$$
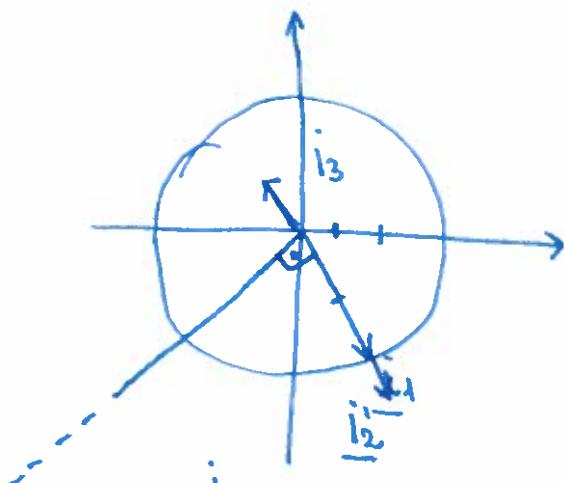
$$i_3(t) = \sqrt{2} \sin(100t + \frac{3\pi}{4})$$



$$\underline{V_{C_2}} = \underline{Z_{C_2}} \cdot \underline{i_2} = -100j \cdot \frac{3\sqrt{2}}{2}(1-j) = -\frac{300}{2}\sqrt{2}(-1-j) \\ = 300 \cdot 2 j^{\frac{5\pi}{4}}$$

$$S_{\text{geom}} = \underline{E_1} \cdot \underline{i_1}^* = -120\sqrt{2}j \cdot \sqrt{2}(1+j) = 240(1-j)$$

$$S_{\text{rec}} = \underline{Z_1} \cdot i_1^2 + \underline{Z_2} i_2^2 + \underline{Z_3} i_3^2 \\ = 60 \cdot 2^2 + -40j \cdot 3^2 + 120j \cdot 1^2 \\ = 240 - 360j + 120j = \underbrace{240}_{P} - \underbrace{240j}_{Q}$$

