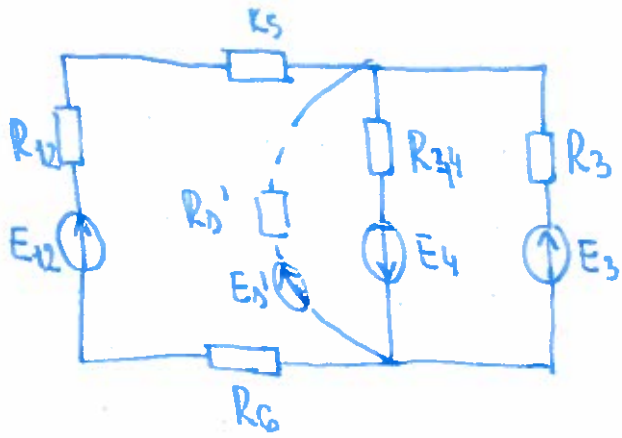


$R (\Omega)$	$i (A)$	$E (V)$
$R_1 = 10\Omega$	$i_1 = 9$	$E_1 = 135$
$R_2 = 10\Omega$	$i_2 = 7$	$E_2 = 25$
$R_3 = 10\Omega$	$i_3 = 7$	$E_3 = 85$
$R_4 = 10\Omega$	$i_4 = 9A$	$E_4 = 75$
$R_5 = 10\Omega$	$i_5 = 2$	
$R_6 = 5\Omega$	$i_6 = 2$	




$$R_{12} = \frac{R_1}{2} = 5 \Omega$$

$$E_{12} = \frac{E_1 G_1 - E_2 G_2}{G_1 + G_2} = \frac{E_1 R_2 - E_2 R_1}{R_1 + R_2}$$

$$= \frac{135 \cdot 10 - 25 \cdot 10}{2 \cdot 10} = 55 \text{ V}$$

$$R_{D'} = R_5 + R_6 + R_{12} = 5 + 5 + 10 = 20 \Omega$$

$$E_{D'} = E_{12} = 55 \text{ V}$$

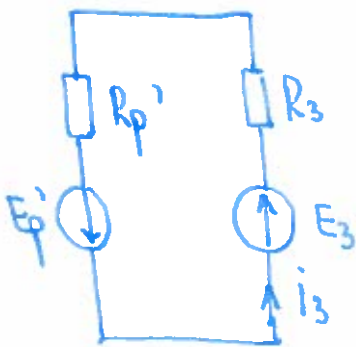


$$R_{p'} = \frac{R_{D'} \cdot R_4}{R_{D'} + R_4} = \frac{20 \cdot 10}{30} = \frac{20}{3} \Omega$$

$$E_{p'} = \frac{-E_{D'} G_{D'} + E_4 G_4}{G_{D'} + G_4} = \frac{-E_{D'} R_4 + E_4 R_{D'}}{R_4 + R_{D'}}$$

$$E_{p'} = \frac{-55 \cdot 10 + 75 \cdot 20}{30} = \frac{95}{3}$$
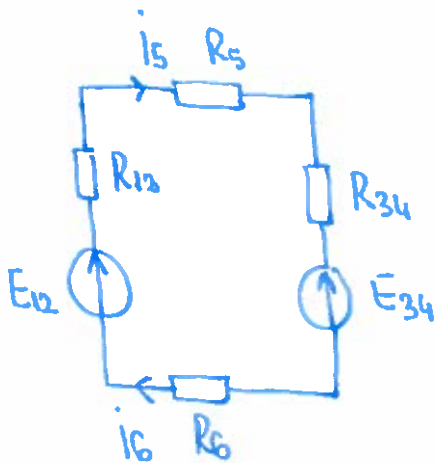
$$i_3 = \frac{E_3 + E_{p'}}{R_{p'} + R_3} = \frac{85 + \frac{95}{3}}{10 + \frac{20}{3}} = \frac{350}{50} = 7 \text{ A}$$



$$i_5 = i_6 = \frac{E_{12} - E_{34}}{R_{12} + R_5 + R_6 + R_{34}} = \frac{55 - 5}{5 + 15 + 5 + 5} = \frac{50}{25} = 2 \text{ A}$$

$$i_5 = i_6 = \frac{E_e}{R_e} = \frac{50}{25} = 2 \text{ A}$$

$$i_2 = ?$$

$$i_4 = ?$$

$i_2$

From the downside node,  $K_2$  says:

$$i_2 + i_6 = i_1 \Rightarrow i_2 = i_1 - i_6 = 9 - 2 = 7A$$

$i_4$

$$i_4 = i_6 + i_3 = 2 + 7 = 9A$$

$$U_{AB} = -R_1 i_1 + E_1 \\ = R_2 i_2 - E_2$$

$$U_{BA} = R_1 i_1 - E_1 \\ = E_2 - R_2 i_2$$

$$U_{AB} =$$

$$U_{BA} =$$

$$U_{CB} =$$

$$U_{BC} =$$

$$U_{CB} =$$

$$U_{BC} =$$