
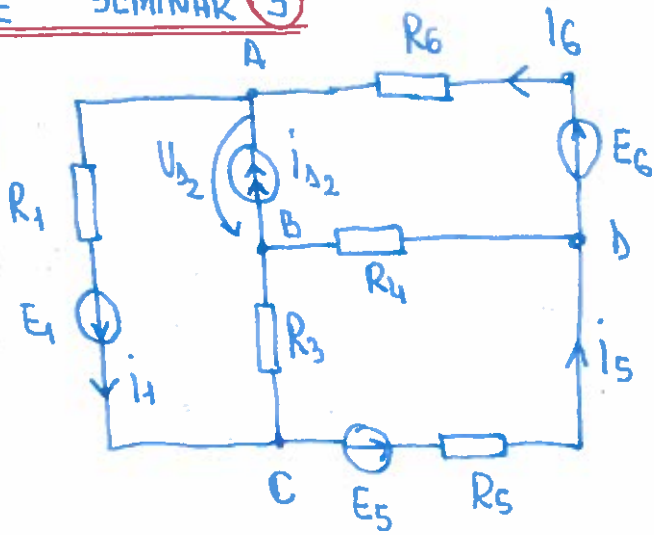


1

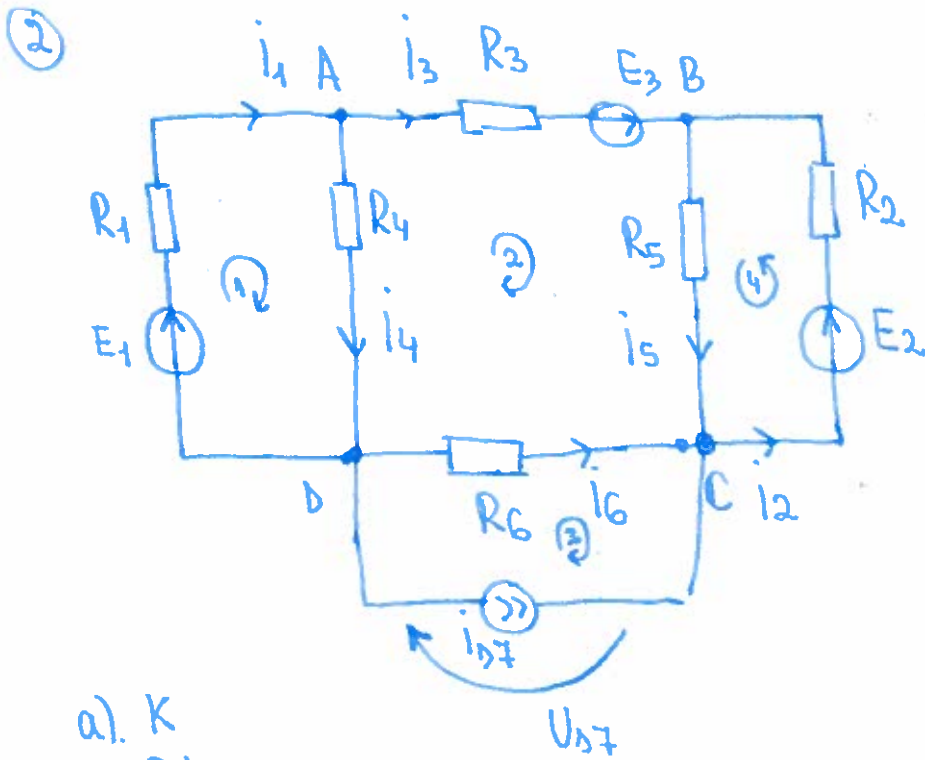

$R(\Omega)$	$i(A)$	$E(V)$
$R_1 = 5$	$i_2 = 1$	$E_1 = 8$
$R_3 = 4$		
$R_4 = 4$		
$R_5 = 3$		$E_5 = 24$
$R_6 = 5$		$E_6 = 5$



$R(\Omega)$	i (A)	E (V)
$R_1 = 4$	$i_1 = 5/4$	$E_1 = 8$
$R_2 = 3$	$i_2 = 0$	$E_2 = 6$
$R_3 = 3$	$i_3 = 1$	$E_3 = 18$
$R_4 = 12$	$i_4 = 1/4$	
$R_5 = 6$	$i_5 = 1$	
$R_6 = 4$	$i_6 = 3$	
	$i_7 = 2$	$U_{D7} = 12$

- a). K
 b). P.b.
 c). AB, BC, CD, AC, BD

$N: 4 \Rightarrow 3 \text{ eq } K_1$

$B - N + 1 = 7 - 4 + 1 = 4 \text{ loops} \Rightarrow 4 \text{ eq } K_2$

$$\left\{ \begin{array}{l} \textcircled{1}: i_1 R_1 + i_4 R_4 = E_1 \\ \textcircled{2}: -i_6 R_6 - i_4 R_4 + i_3 R_3 + i_5 R_5 = E_3 \\ \textcircled{3}: i_6 R_6 + U_{D7} = 0 \\ \textcircled{4}: i_2 R_2 + i_5 R_5 = E_2 \\ \textcircled{A}: i_1 = i_3 + i_4 \\ \textcircled{B}: i_5 = i_2 + i_3 \\ \textcircled{D}: i_4 = i_1 + i_6 + i_7 \Rightarrow i_6 = i_4 - i_1 - i_7 = -i_3 - 2 \end{array} \right.$$

$$\left\{ \begin{array}{l} (i_3 + i_4) \cdot 4 + i_4 \cdot 12 = 8 \\ -4(-i_3 - 2) - 12i_4 + 3i_3 + 6i_5 = 18 \\ +4(-i_3 - 2) + U_{D7} = 0 \\ 3i_2 + 6(i_2 + i_3) = 6 \end{array} \right. \Leftrightarrow \left\{ \begin{array}{l} 4i_3 + 16i_4 = 8 + 6i_2 \\ 7i_3 - 12i_4 + 6i_5 = 10 \\ -4i_3 + U_{D7} = 8 \\ 9i_2 + 6i_3 = 6 \end{array} \right.$$

$$\begin{cases} i_3 + 4i_4 = 2 \\ 2i_2 + 13i_3 - 12i_4 = 10 \\ -4i_3 + U_{\Delta 7} = 8 \\ 3i_2 + 2i_3 = 2 \quad | \cdot 2 \end{cases} \Rightarrow \begin{cases} i_3 + 4i_4 = 2 & | \cdot 3 \\ 9i_3 - 12i_4 = 6 & | + \\ -4i_3 + U_{\Delta 7} = 8 \end{cases}$$

$$12i_3 = 12 \Rightarrow i_3 = 1 \text{ A} \Rightarrow U_{\Delta 7} = 12 \text{ V}$$

$$i_4 = \frac{3}{12} = \frac{1}{4} \text{ A}$$

$$i_2 = 0 \text{ A}$$


b). P. balance:

$$P_{gen} = P_{consumed} \Rightarrow i_1 E_1 + i_2 E_2 + i_3 E_3 + U_{\Delta 7} \cdot i_{\Delta 7} = 10 + 0 + 18 + 24 = 52$$

$$P_{ruce} = i_1^2 R_1 + R_3 i_3^2 + R_4 i_4^2 + R_5 i_5^2 + R_6 i_6^2$$

$$= \frac{25}{9} \cdot 4 + 1 \cdot 3 + \frac{1}{16} \cdot 12 + 6 \cdot 1 + 4 \cdot 9$$
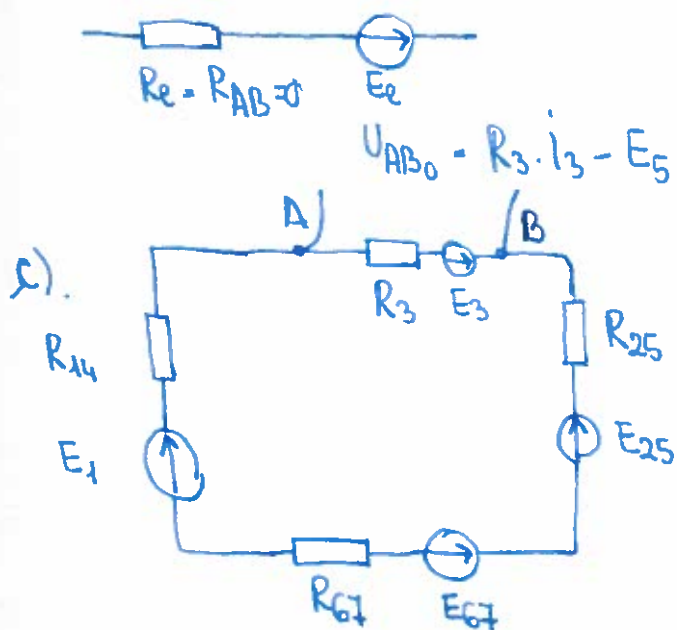
$$= \overset{4)}{\frac{100}{9}} + 3 + \overset{9)}{\frac{3}{4}} + 6 + 36 = 45 + \frac{427}{36} = 52 \text{ W}$$



$$R_{14} = \frac{R_1 R_4}{R_1 + R_4} = \frac{4 \cdot 12}{16} = 3 \Omega$$

$$E_{14} = \frac{E_1 R_4}{R_1 + R_4} = \frac{8 \cdot 12}{16} = 6 \text{ V}$$

$$R_{67} = R_6 = 4 \Omega \quad E_{25} = \frac{E_2 \cdot R_5}{R_2 + R_5} = 4 \text{ V}$$

$$E_{67} = R_6 \cdot i_{\Delta 7} = 8 \text{ V}$$

$$R_{25} = \frac{R_2 R_5}{R_2 + R_5} = \frac{18}{9} = 2 \Omega$$

$$E_s = E_{67} + E_{25} - E_{14} = 6V$$

$$R_s = R_{14} + R_{67} + R_{25} = 3 + 4 + 2 = 9 \Omega$$

$$R_{eq} = \frac{R_s \cdot R_3}{R_s + R_3} = \frac{9 \cdot 3}{12} = \frac{9}{4} \Omega$$

$$E_{eq} = \frac{\frac{E_3}{R_3} + \frac{E_s}{R_s}}{\frac{1}{R_3} + \frac{1}{R_s}} = \frac{E_3 R_s + E_s R_3}{R_3 + R_s} = 15V$$

Homework: find out for the rest of the cases