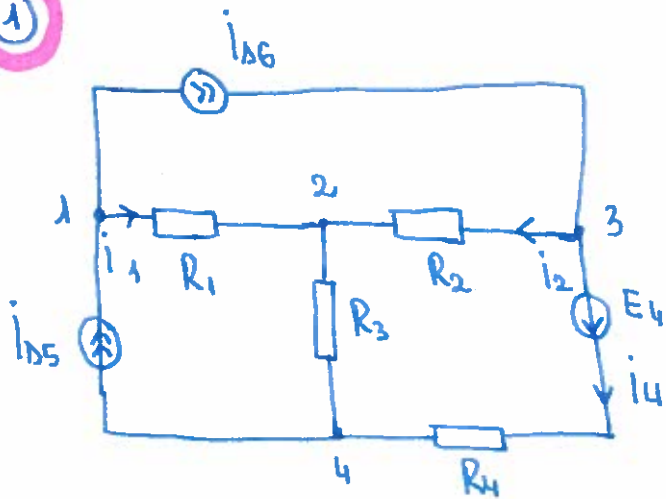


①




$R_1 = 1$		
$R_2 = 1$		
$R_3 = 1$		
$R_4 = 1/2$		E_4
	$i_{D5} = 3$	
	$i_{D6} = 8$	

$V_4 = 0$

$$\begin{cases} G_{11}V_1 + G_{12}V_2 + G_{13}V_3 = J_{sc1} \\ G_{21}V_1 + G_{22}V_2 + G_{23}V_3 = J_{sc2} \\ G_{31}V_1 + G_{32}V_2 + G_{33}V_3 = J_{sc3} \end{cases}$$

②

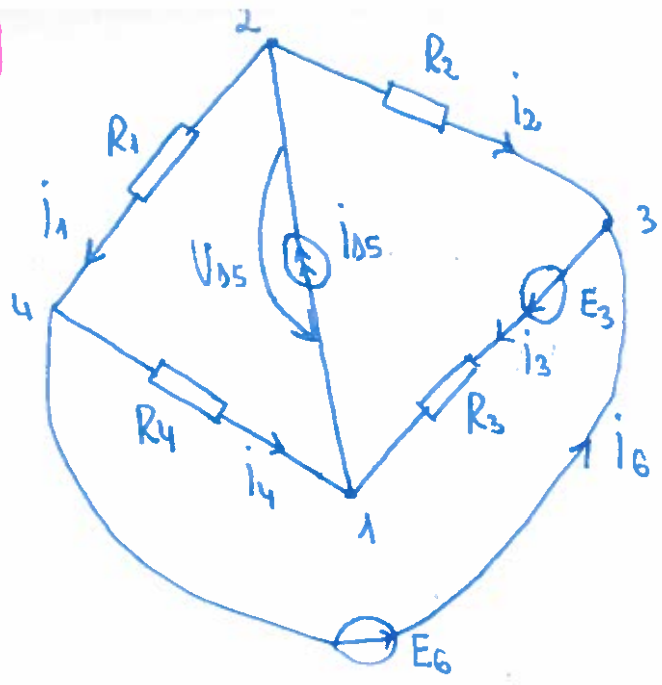

R(Ω)	i(A)	E(V)
R ₁ = 1	2	
R ₂ = 1	1	
R ₃ = +2	2	E ₃ = 2
R ₄ = 1	1	
	I _{N5} = 3	V _{N5} = 3
	1	E ₆ = 1

$V_4 = 0$
 $V_3 - V_4 = E_6$
 $V_3 = E_6 = 1$

$$\begin{cases} G_{11}V_1 + G_{12}V_2 + G_{13}V_3 = I_{Nc1} \\ G_{21}V_1 + G_{22}V_2 + G_{23}V_3 = I_{Nc2} \end{cases}$$

$$G_{11} = \frac{1}{R_4} + \frac{1}{R_3} = \frac{3}{2}$$

$$G_{22} = \frac{1}{R_1} + \frac{1}{R_2} = 2$$

$G_{12} = G_{21} = 0$
 $G_{13} = -\frac{1}{R_3} = -\frac{1}{2}$
 $G_{23} = -\frac{1}{R_2} = -1$

$I_{Nc1} = \frac{E_3}{R_3} - I_{N5} = 1 - 3 = -2$
 $I_{Nc2} = I_{N5} = 3$

$$\begin{cases} \frac{3}{2}V_1 - \frac{1}{2} \cdot 1 = -2 \\ 2V_2 - 1 = 3 \end{cases}$$

$3V_1 = -3 \Rightarrow V_1 = -1$
 $V_2 = 2$

$V_2 - V_4 = R_1 I_1 \Rightarrow I_1 = \frac{2}{1} = 2A$
 $V_2 - V_3 = R_2 I_2 \Rightarrow I_2 = \frac{2-1}{1} = 1A$
 $V_3 - V_1 = R_3 I_3 - E_3 \Rightarrow I_3 = \frac{1+1+2}{2} = 2A$
 $V_1 - V_4 = -R_4 I_4 \Rightarrow I_4 = \frac{-1}{-1} = 1A$

$V_2 - V_1 = V_{N5}$
 $V_{N5} = 3V$
 $I_6 + I_2 = I_3 \Rightarrow I_6 = 1A$


POWER BALANCE

$$P_{\text{src}} = P_{\text{gen}}$$

$$P_{\text{src}} = R_1 i_1^2 + R_2 i_2^2 + R_3 i_3^2 + R_4 i_4^2 = 4 + 1 + 8 + 1 = 14 \text{ W}$$

$$P_{\text{gen}} = I_3 E_3 + U_{S5} \cdot I_{S5} + I_6 E_6 = 4 + 9 + 1 = 14 \text{ W}$$

③

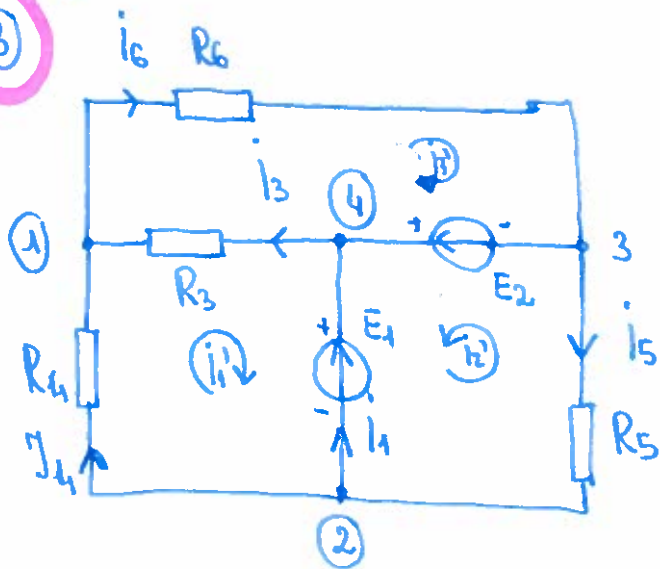

$R(\Omega)$	$i(\text{A})$	$E(\text{V})$
$R_1 =$	4	$E_1 = 4$
	-2	$E_2 = 2$
$R_3 = 1$	2	
$R_4 = 1$	-2	
$R_5 = 1$	2	
$R_6 = 1$	0	

$$V_4 = 0$$

$$G_{11} V_1 + G_{12} V_2 + G_{13} V_3 = I_{\text{src}1}$$

$$G_{11} = \frac{1}{R_4} + \frac{1}{R_3} + \frac{1}{R_6} = 3$$

$$G_{12} = -\frac{1}{R_4} = -1$$

$$I_{\text{src}1} = 0$$

$$G_{13} = -\frac{1}{R_6} = -1$$

$$V_3 - V_4 = -E_2 \Rightarrow V_3 = -2$$

$$V_2 - V_4 = -E_1 \Rightarrow V_2 = -4$$

$$3V_1 + 4 + 2 = 0$$

$$V_1 = -2$$

$$V_2 - V_1 = I_4 R_4 \Rightarrow I_4 = \frac{-4 + 2}{1} = -2 \text{ A}$$

$$V_3 - V_2 = I_5 R_5 \Rightarrow I_5 = \frac{-2 + 4}{1} = 2 \text{ A}$$

$$V_1 - V_3 = I_6 R_6 \Rightarrow I_6 = \frac{-2 + 2}{1} = 0 \text{ A}$$

$$V_4 - V_1 = I_3 R_3 \Rightarrow I_3 = 2 \text{ A}$$

$$I_6 = I_2 + I_5 \Rightarrow I_2 = I_6 - I_5 = -2 \text{ A}$$

$$I_5 = I_1 + I_4 \Rightarrow I_1 = 4$$

$$\text{Power Balance: } P_{\text{src}} = P_{\text{gen}}$$

$$P_{\text{src}} = R_3 i_3^2 + R_4 i_4^2 + R_5 i_5^2 + R_6 i_6^2 = 4 + 4 + 4 = 12 \text{ W}$$

$$P_{\text{gen}} = E_2 i_2 + E_1 i_1 = 16 - 4 = 12 \text{ W}$$

Kirchoff , Loop Current

Kirchoff:

$$\left\{ \begin{array}{l} i_4 R_4 - i_3 R_3 = -E_1 \\ -R_5 i_5 = E_2 - E_1 \\ i_3 R_3 + i_6 R_6 = E_2 \end{array} \right.$$

Loop Current:

$$l_1: b_4, b_3$$

$$l_2: b_5$$

$$l_3: b_3, b_6$$

$$\left\{ \begin{array}{l} R_{11} i_1' + R_{12} i_2' + R_{13} i_3' = E_1' \\ R_{21} i_1' + R_{22} i_2' + R_{23} i_3' = E_2' \\ R_{31} i_1' + R_{32} i_2' + R_{33} i_3' = E_3' \end{array} \right.$$

$$R_{11} = R_4 - R_3 = 0$$

$$R_{12} = R_{21} = 0$$

$$R_{22} = -R_5 = -1$$

$$R_{13} = R_{31} = -R_3 = -1$$

$$R_{33} = R_6 = 1$$

$$\left\{ \begin{array}{l} E_1' = -E_1 = -4 \\ E_2' = E_2 - E_1 = -2 \\ E_3' = E_2 = 2 \end{array} \right.$$

