

	$R(\Omega)$	$I(A)$	$E(V)$
b_1		$i_1 = 3$	$E_1 = 30$
b_2	$R_2 = 15$	$i_2 = 2$	
b_3		$i_{33} = 1$	$U_{33} = -30$
b_4	$R_4 = 10$	$i_4 = 1$	$E_4 = 20$
b_5		$i_{55} = 2$	$U_{55} = -10$
b_6	$R_6 = 10$	$i_6 = 1$	
b_7	$R_7 = 20$	$i_7 = 2$	$E_7 = 50$

$N = 4$
 $B = 7$
 $L = B - N + 1 = 4$

Calculate $i_1, i_2, i_4, i_6, i_7, U_{33}, U_{55}$ using:

- Kirchoff equation method
- Loop currents method
- Node potential method
- U_1, U_2, U_4, U_6, U_7
- Power balance?

a) $K_I \rightarrow (m-1)$ times $K_{II} (B-N+1)$ times

$$\begin{cases} N_1: & i_{33} + i_2 = i_1 \Rightarrow i_1 = i_2 + 1 \\ N_4: & i_{55} + i_6 = i_4 + i_7 \Rightarrow i_6 = i_4 + i_7 - 2 = i_7 - 2 + 1 = i_7 - 1 \\ N_3: & i_{55} = i_{33} + i_4 \Rightarrow i_4 = i_{55} - i_{33} = 2 - 1 = 1A \end{cases}$$

$$\begin{array}{l}
 \textcircled{\text{LI}} \\
 \textcircled{\text{LII}} \\
 \textcircled{\text{LIII}} \\
 \textcircled{\text{LIV}}
 \end{array}
 \left\{ \begin{array}{l}
 R_2 i_2 = E_1 \\
 R_2 i_2 + U_{s3} + R_4 i_4 + R_6 i_6 = E_4 \\
 R_4 i_4 - U_{s5} = E_4 \\
 R_6 i_6 + R_7 i_7 = E_7
 \end{array} \right.
 \quad
 \left\{ \begin{array}{l}
 15 i_2 = 30 \Rightarrow i_2 = 2A \Rightarrow i_1 = 3A \\
 15 \cdot 2 + U_{s3} + 10 \cdot 1 + 10(i_7 - 1) = 20 \\
 10 \cdot 1 - U_{s5} = 20 \Rightarrow U_{s5} = -10V \\
 10(i_7 - 1) + 20 i_7 = 50
 \end{array} \right.$$

$$\left. \begin{array}{l}
 U_{s3} + 10 i_7 = -10 \\
 30 i_7 = 60 \Rightarrow i_7 = 2A
 \end{array} \right\} \Rightarrow \begin{array}{l}
 U_{s3} = -10 - 20 = -30V \\
 i_6 = 2 - 1 \Rightarrow i_6 = 1A
 \end{array}$$

b). Loop Current Method (LC)

There are two current sources $i_{s3}, i_{s5} \Rightarrow$ two restrictions
 (We have to choose the loops such that i_{s3}, i_{s5} not to be on a common branch) \Rightarrow we can keep the same choice like for a).

$i_1', i_2', i_3', i_4' \rightarrow$ loop currents

$$\text{LI} \quad R_{11} i_1' + R_{12} i_2' + R_{13} i_3' + R_{14} i_4' = E_{L1}$$

$$\text{LII} \quad i_2' = -i_{s3} = -1A \quad \textcircled{*} \text{ it replaces the eq. corresponding to method L.C.}$$

$$\text{LIII} \quad R_{31} i_1' + R_{32} i_2' + R_{33} i_3' + R_{34} i_4' = E_{L3}$$

$$\textcircled{\text{LIV}} \quad i_4' = i_{s5} = 2A \quad \textcircled{*}$$

$$R_{11} = R_2 = 15 \quad (\text{total resistance loop I})$$

$$R_{12} = +R_2 = 15 \quad (\text{common } R \text{ between LI and LII})$$

$$R_{13} = 0 \quad (\text{common } R: \text{LI, LIII})$$

$$R_{14} = 0 \quad (\text{common } R: \text{LI, LIV})$$

$$E_{L1} = E_1 = 30 \quad (\text{total voltage source of LI})$$

$$R_{31} = R_{13} = 0$$

$$R_{32} = +R_6 = 10 \quad (\text{common } R : L_{II}, L_{III})$$

$$R_{34} = 0 \quad (\text{common } R : L_{III}, L_{IV})$$

$$R_{33} = R_6 + R_7 = 30$$

(total resistance loop III)

$$E_{L_3} = E_7 = 50 \quad (\text{total voltage source of III})$$

$$\begin{cases} 15i_1' + 15(-1) = 30 \Rightarrow i_1' = 3A \\ 0 + 10(-1) + 30i_3' + 0 = 50 \Rightarrow i_3' = 2A \end{cases}$$

Real currents calculation

$$I_1 = I_1' = 3A$$

$$I_2 = i_1' + i_2' = 3 - 1 = 2A$$

$$I_4 = i_2' + i_4' = -1 + 2 = 1A$$

$$I_6 = i_2' + i_3' = -1 + 2 = 1A$$

$$I_7 = i_3' = 2A$$

In order to calculate the unknown voltages U_{33} & U_{55} , we have to go back to KVL on the loop that contain these

branches : loop IV : $R_4 i_4 - U_{55} = E_4$

$$U_{55} = R_4 i_4 - E_4 = -10V$$

loop V : $R_2 i_2 + U_{33} + R_4 i_4 + R_6 i_6 = E_7$

$$U_{33} = E_7 - R_2 i_2 - R_4 i_4 - R_6 i_6 = 30V$$

d). $U_1 = -E_1 = -30V \quad (U_{01})$

$$U_2 = R_2 i_2 = 30V$$

$$U_4 = R_4 i_4 - E_4 = -10V = U_{55}$$

$$U_6 = R_6 i_6 = 10V$$

$$U_7 = R_7 i_7 - E_7 = -10V = -U_6$$

c). Node Potential Method (NP)

With respect to this method we have also a restriction due to the presence of the ideal voltage source E_m (without any other element on that branch) \Rightarrow We have to choose the reference node for the potential to be one of the terminals of that branch \rightarrow node 1 or 2

Let's suppose that the reference potential $V_2 = 0$.

Then, for the other terminal, we don't write the eq. corresponding to NP method, but we write directly:

$$V_2 - V_1 = E_1 \Rightarrow V_1 = -E_1 \Rightarrow V_1 = -30V$$

For the other 2 nodes, we apply the method: $G = \text{conductance}$

$$\begin{cases} \textcircled{3} & G_{31}V_1 + G_{32}V_2 + G_{33}V_3 + G_{34}V_4 = i_{sc3} \\ \textcircled{4} & G_{41}V_1 + G_{42}V_2 + G_{43}V_3 + G_{44}V_4 = i_{sc4} \end{cases}$$

$i \neq j$ common bet 2 nodes (≤ 0) $i = j$ total c. of the node:

$$G_{31} = 0 \quad \left(\frac{1}{\infty} \text{ from branch 3} \right)$$

$$G_{33} = \frac{1}{\infty} + \frac{1}{R_4} + \frac{1}{\infty} = \frac{1}{R_4} = \frac{1}{10}$$

$$G_{34} = -\left(\frac{1}{R_4} + \frac{1}{\infty} \right) = -\frac{1}{R_4} = -\frac{1}{10}$$

$$i_{sc3} = -i_{s3} + i_{s5} - \frac{E_4}{R_4} = -1 + 2 - \frac{20}{10} = -1$$

$$i_{sc4} = \frac{E_4}{R_4} + \frac{E_7}{R_7} - i_{s5} = \frac{20}{10} - 2 + \frac{50}{20} = \frac{5}{2}$$

$$G_{41} = 0 \quad (\text{no connection bet. } n_1 \text{ \& } n_4)$$

$$G_{43} = G_{34} = -\frac{1}{R_4} = -\frac{1}{10}$$

$$G_{44} = \frac{1}{\infty} + \frac{1}{R_4} + \frac{1}{R_8} + \frac{1}{R_7} = \frac{1}{10} + \frac{1}{10} + \frac{1}{20} = \frac{3}{10}$$

$$\begin{cases} \frac{1}{10}V_3 - \frac{1}{10}V_4 = -1 \\ -\frac{1}{10}V_3 + \frac{5}{20}V_4 = \frac{5}{2} \end{cases}$$

$$\Leftrightarrow \begin{cases} V_3 - V_4 = -10 \quad | \cdot 2 \\ -2V_3 + 5V_4 = 50 \quad | + \end{cases}$$

$$\begin{aligned} 3V_4 &= 30 \Rightarrow V_4 = 10 \\ V_3 &= 0 \end{aligned}$$

We calculate the real quantities using Ohm's law on each branch:

$$V_2 - V_1 = R_2 i_2 \Rightarrow i_2 = \frac{V_2 - V_1}{R_2} = 2 \text{ A}$$

$$V_1 - V_3 = U_{s3} = -30 \text{ V}$$

$$V_2 - V_4 = R_7 i_7 - E_7 \Rightarrow i_7 = \frac{V_2 - V_4 + E_7}{R_7} = 2 \text{ A}$$

$$V_4 - V_2 = R_6 i_6 \Rightarrow i_6 = \frac{V_4 - V_2}{R_6} = 1 \text{ A}$$

$$V_3 - V_4 = R_4 i_4 - E_4 \Rightarrow i_4 = \frac{V_3 - V_4 + E_4}{R_4} = 1 \text{ A}$$

$$V_3 - V_4 = U_{s5} = -10 \text{ V}$$

$$i_1 + i_6 = i_2 + i_7 \Rightarrow i_1 = i_2 + i_7 - i_6 = 3 \text{ A}$$

2). Power balance: $P_c = P_g \text{ (W)}$


$$P_c = R_2 i_2^2 + R_4 i_4^2 + R_6 i_6^2 + R_7 i_7^2 = 60 + 10 + 10 + 80 = 160 \text{ W}$$

$$P_g = E_1 i_1 + U_{s3} i_{s3} + E_4 i_4 + U_{s5} i_{s5} + E_7 i_7 = 90 - 30 + 20 - 20 + 100 = 160 \text{ W}$$

Review on all methods

2

Let's consider the following circuit:

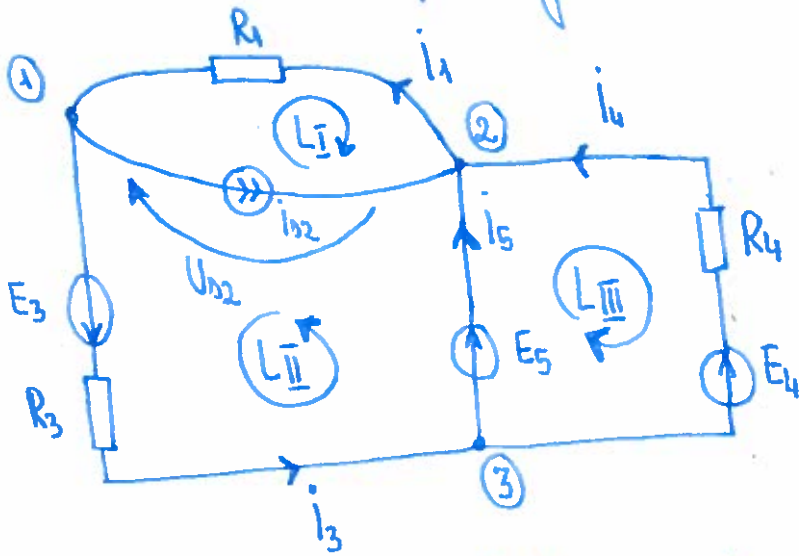

$R (\Omega)$	$i (A)$	$E (V)$
$R_1 = 4$	$i_1 = 5A$	
	$i_2 = 3$	$U_{o2} = 20$
$R_3 = 5$	$i_3 = 2$	$E_3 = 20$
$R_4 = 4$	$i_4 = -2$	$E_4 = 2$
	$i_5 = 4$	$E_5 = 10$

Apply: a). Kirchhoff method b). Loop Current Method c). Node Potential Method
 d). $i_1, U_{o2}, i_3, i_4, i_5$ e) Verify the results using Power Balance

a). $N = 3$ nodes
 $B = 5$ branches
 $L = B - N + 1 = 3$ loops

(K1) $\begin{cases} i_1 = i_2 + i_3 = i_3 + 3 \\ i_3 = i_4 + i_5 \Rightarrow i_5 = i_3 - i_4 \end{cases}$


(K2) $\begin{cases} U_{o2} - R_1 i_1 = 0 \\ R_3 i_3 + U_{o2} = E_5 + E_3 \\ -R_4 i_4 = E_5 - E_4 \end{cases}$

$\begin{cases} U_{o2} - 4(i_3 + 3) = 0 \\ +U_{o2} + 5i_3 = 30 \end{cases} \Rightarrow \begin{cases} -9i_3 = -18 \\ i_3 = 2A \end{cases}$

$i_1 = 5A \quad -4i_4 = 8 \Rightarrow i_4 = -2A \quad i_5 = 2 + 2 = 4A$

$U_{o2} = R_1 i_1 = 4 \cdot 5 = 20V$

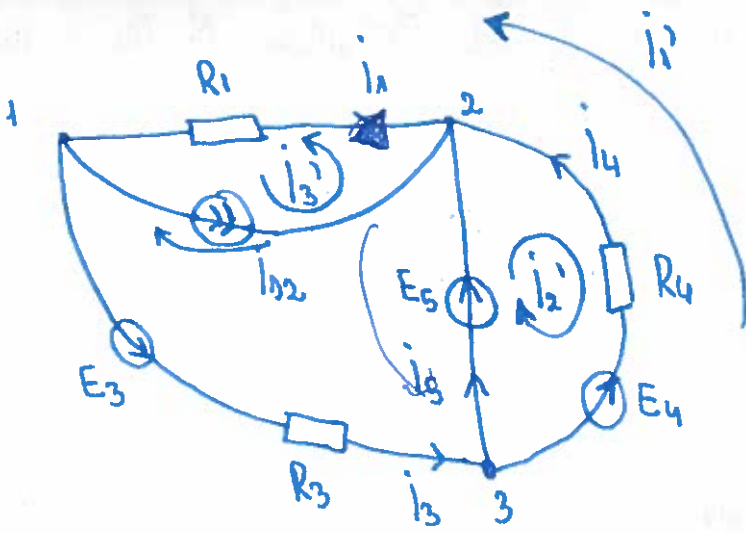b). The presence of $U_{o2} \Rightarrow$ restriction \Rightarrow the branch b_2 must not be "common" branch.



$$l_3: \underline{b_1}, b_2$$

$$l_2: b_4, b_5$$

$$l_1: \underline{b_1}, b_3, \underline{b_4}$$

$$\begin{cases} l_3: i_3' = i_{s2} = 3A \\ l_1: R_{11}i_1' + R_{12}i_2' + R_{13}i_3' = E_1' \\ l_2: R_{21}i_1' + R_{22}i_2' + R_{23}i_3' = E_2' \end{cases}$$

$$\begin{cases} R_{11} = R_1 + R_3 + R_4 = 13 \\ R_{12} = R_{21} = -R_4 = -4 \\ R_{13} = R_1 = 4 \\ R_{22} = R_4 = 4 \\ R_{23} = 0 \end{cases}$$

$$E_1' = E_3 + E_4 = 22V$$

$$E_2' = E_5 - E_4 = 8V$$

$$\begin{cases} 13i_1' - 4i_2' + 4 \cdot 3 = 22 \\ -4i_1' + 4i_2' = 8 \end{cases}$$

$$9i_1' / + 12 = 30 \quad (4) \Rightarrow i_1' = 2A$$

$$i_2' = 4A$$

$$i_1 = i_1' + i_3' = 2 + 3 = 5A$$

$$i_3 = i_1' = 2A$$

$$i_4 = i_1' - i_2' = 2 - 4 = -2A$$

$$i_5 = i_2' = 4A$$

$$R_3 i_3 + U_{s2} = E_3 + E_5$$

$$U_{s2} = 10 + 20 - 10 = 20V$$

c). The presence of $E_5 \Rightarrow$ restriction \Rightarrow one of the terminals of the branch b_5 must be considered reference node of potential 0.

Let's take $V_3 = 0$

Then $V_2 - V_3 = E_5$

$$V_2 = E_5 = 10$$

\Leftarrow For node 2 we don't write anymore the eq. of the method but we write directly Ohm's law

The only equation that remains is:

$$\rightarrow G_{11} V_1 + G_{12} V_2 = I_{sc1} \Leftrightarrow \begin{cases} G_{11} = \frac{1}{R_1} + \frac{1}{R_3} = \frac{1}{4} + \frac{1}{5} = \frac{9}{20} \\ G_{12} = -\frac{1}{R_1} = -\frac{1}{4} \\ I_{sc1} = -\frac{E_3}{R_3} - I_{s2} = -4 - 3 = -7 \end{cases}$$

$$\frac{9}{20} V_1 - \frac{1}{4} \cdot 10 = -7$$

$$9V_1 - 50 = -140 \Rightarrow V_1 = -10$$

$$V_2 - V_1 = R_1 i_1 \Rightarrow i_1 = \frac{V_2 - V_1}{R_1} = \frac{10 - (-10)}{4} = 5A$$

$$V_2 - V_1 = U_s \Rightarrow U_s = 20V$$

$$V_1 - V_3 = R_3 i_3 - E_3 \Rightarrow i_3 = \frac{V_1 - V_3 + E_3}{R_3} = \frac{-10 + 20}{5} = 2A$$

$$V_3 - V_2 = R_4 i_4 - E_4 \Rightarrow i_4 = \frac{V_3 - V_2 + E_4}{R_4} = \frac{-10 + 20}{4} = 2.5A$$

For I_5 we apply K \bar{I} $i_3 = i_5 + i_4 \Rightarrow i_5 = i_3 - i_4 = 2 - 2.5 = -0.5A$


d). Power balance:

$$P_{gen} = P_{rec} \Leftrightarrow$$

$$R_1 i_1^2 + R_3 i_3^2 + R_4 i_4^2 = U_s i_5 + E_3 i_3 + E_4 i_4 + E_5 i_5$$

$$100 + 20 + 16 = 60 + 40 - 4 + 40 \Rightarrow 136W = 136W$$

③ Let's consider the following circuit:

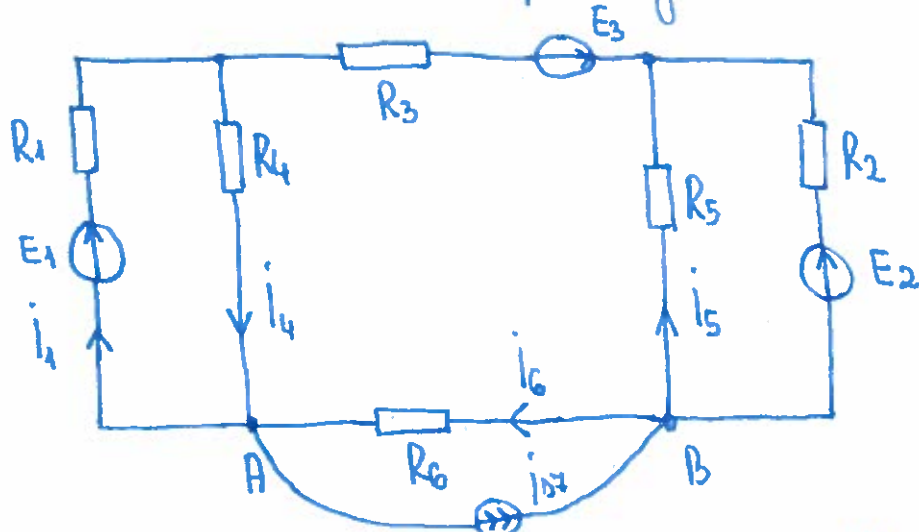

$$R_1 = R_6 = 4\Omega$$

$$R_2 = R_3 = 3\Omega$$

$$R_4 = 12\Omega \quad R_5 = 6\Omega$$

$$E_1 = 8V \quad E_2 = 6V$$

$$E_3 = 18V \quad J_{07} = 2A$$

a) Using Thevenin theorem calculate the current J_6

$$E_{14} = \frac{\frac{E_1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_4}} = \frac{E_1 R_4}{R_1 + R_4} = \frac{8 \cdot 12}{4 + 12} = \frac{8 \cdot 12}{16} = 6V$$

$$R_{14} = \frac{R_1 R_4}{R_1 + R_4} = \frac{4 \cdot 12}{16} = 3\Omega$$

$$E_{25} = \frac{\frac{E_2}{R_2}}{\frac{1}{R_2} + \frac{1}{R_5}} = \frac{E_2 R_5}{R_2 + R_5} = \frac{6 \cdot 6}{3 + 6} = 4V$$

$$R_{25} = \frac{R_2 R_5}{R_2 + R_5} = \frac{3 \cdot 6}{9} = 2\Omega$$




$$E_{\Delta} = E_{14} + E_3 - E_{25} = 6 + 18 - 4 = 20V$$

$$R_{\Delta} = R_{14} + R_3 + R_{25} = 3 + 3 + 2 = 8\Omega$$

$$R_p = R_{\Delta} = 8\Omega$$


$$E_p = E_{\Delta} + R_{\Delta} \cdot J_{07} = 20 + 8 \cdot 2 = 36V$$
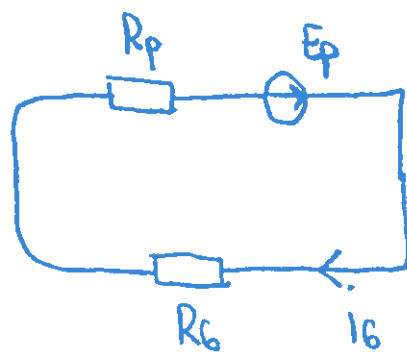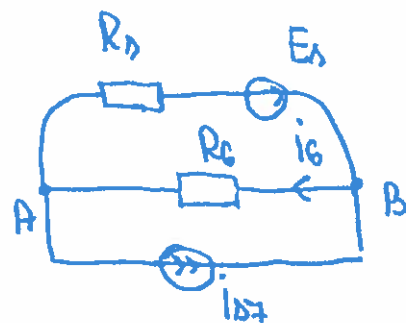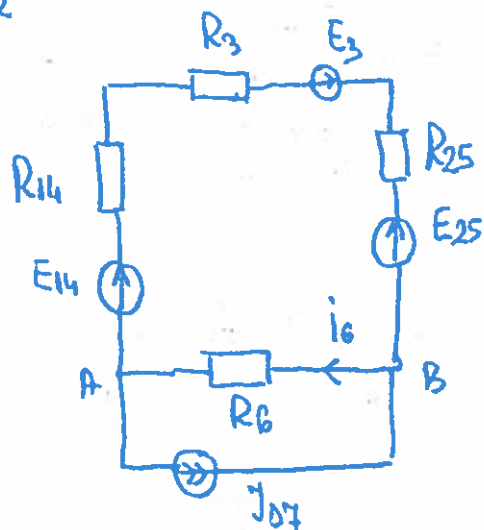
$$i_6 = \frac{E_p}{R_p + R_6} = \frac{36}{8 + 4} = 3A$$



b). Calculate the equivalent Thevenin and Norton generators with respect to the terminals AB

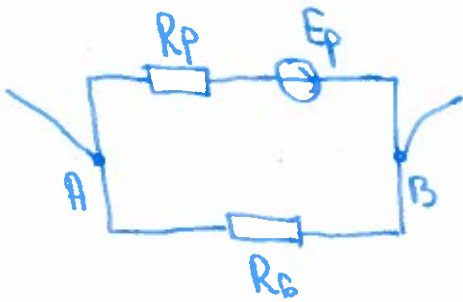
- we can use a). following the same steps



$$R_e = \frac{R_p R_b}{R_p + R_b} = \frac{8 \cdot 4}{8 + 4} = \frac{32}{12} = \frac{8}{3} \Omega$$

$$E_e = \frac{E_p}{\frac{1}{R_p} + \frac{1}{R_b}} = \frac{E_p R_b}{R_p + R_b} = \frac{36 \cdot 4}{8 + 4} = 12V$$
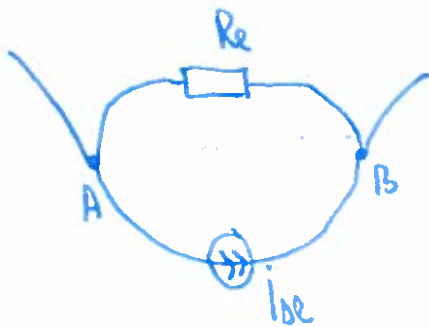
$$\left. \begin{array}{l} E_e = 12V \\ R_e = \frac{8}{3} \Omega \end{array} \right\} \text{(Th. th.)}$$



$$I_{se} = \frac{E_e}{R_e} = \frac{12 \cdot 3}{8 \cdot 2} = \frac{9}{2} A \text{ (Norton gen.)}$$