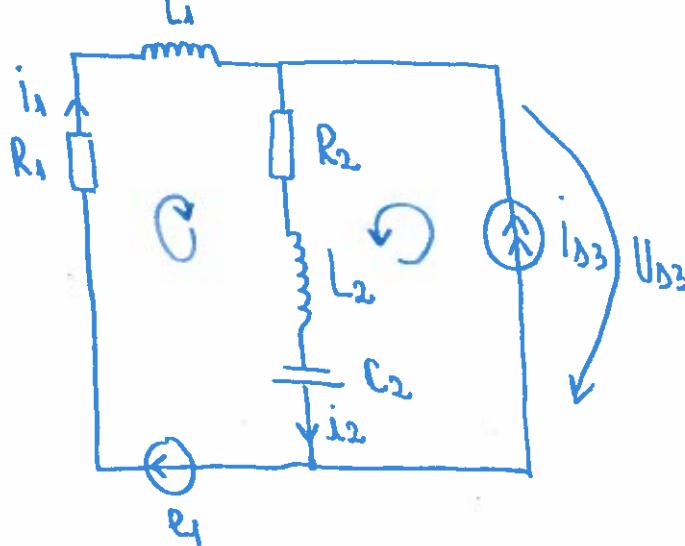


# BE SEMINAR 8

22.11.2010

①



$$e_1(t) = 100\sqrt{2} \sin(100t + \frac{5\pi}{4}) \quad (\text{V})$$

$$I_{B3}(t) = 10\sqrt{2} \sin(100t - \frac{\pi}{3}) \quad (\text{A})$$

$$R_1 = 3\Omega$$

$$R_2 = 2\Omega$$

$$L_1 = 50 \text{ mH}$$

$$L_2 = 30 \text{ mH}$$

$$C_2 = 2 \text{ mF}$$

$$\underline{Z}_1 = ?$$

$$\underline{Z}_2 = ?$$

$$\underline{E}_1 = ?$$

$$\underline{i}_{B3} = ?$$

→ the eq in time domain (PARTIAL sol.)


→ complete resp. one of Mth in complex

a).  $i_2 = i_1 + i_{B3}$

$$\left\{ \underbrace{i_1 R_1 + L_1 \frac{di_1}{dt}}_{\mathcal{U}_{R_1}} + i_2 R_2 + L_2 \frac{di_2}{dt} + \frac{1}{C_2} \int i_2 dt = e_1 \right.$$

$$\left. \mathcal{U}_{R_2} \quad \mathcal{U}_{L_2} \right\}$$
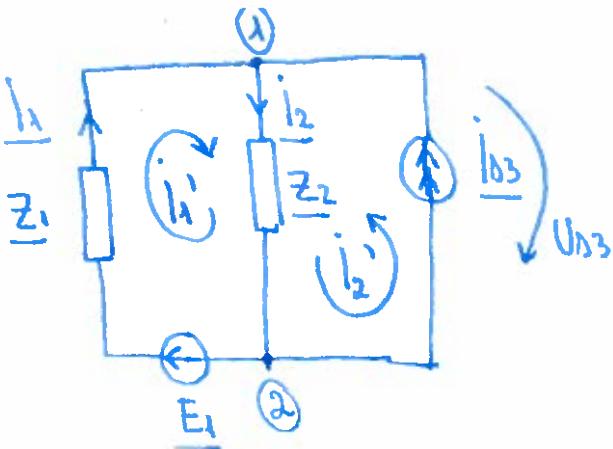
$$\left. i_2 R_2 + L_2 \frac{di_2}{dt} + \frac{1}{C_2} \int i_2 dt - \mathcal{U}_{B3} = 0 \right\}$$



$$\underline{E_1} = E_1 \cdot e^{j \frac{5\pi}{4}} = 100 \cdot e^{j \frac{5\pi}{4}} = 100 \left( \cos \frac{5\pi}{4} + j \sin \frac{5\pi}{4} \right) \\ = 100 \left( -\frac{\sqrt{2}}{2} - j \frac{\sqrt{2}}{2} \right) = -50\sqrt{2} (1+j)$$

$$\underline{Z_1} = R_1 + j\omega L_1 = 3 + j \cdot 100 \cdot 5 \cdot 10^{-2} = 3 + 5j$$

$$\underline{Z_2} = R_2 + j \left( \omega L_2 - \frac{1}{\omega C_2} \right) = 2 + j \left( 3 - \frac{1}{100 \cdot 2 \cdot 10^{-3}} \right) = 2(1-j)$$

$$\underline{I_{B3}} = i_{B3} e^{j - \frac{\pi}{4}} = 10 \cdot e^{j - \frac{\pi}{4}} = 10 \left( \cos \left( -\frac{\pi}{4} \right) + j \sin \left( -\frac{\pi}{4} \right) \right) = 10 \left( \frac{\sqrt{2}}{2} - j \frac{\sqrt{2}}{2} \right) \\ = 5\sqrt{2}(1-j)$$

Kirchhoff:

$$\begin{aligned} \text{I: } & i_2 = i_1 + i_{B3} \\ \text{II: } & \begin{cases} Z_1 i_1 + Z_2 i_2 = E_1 \\ Z_2 i_2 - U_{B3} = 0 \end{cases} \end{aligned}$$

Loop Current:

$$\begin{cases} \underline{Z_{11}} \underline{i_1}' + \underline{Z_{12}} \underline{i_2}' = \underline{E_1}' \\ \underline{i_2}' = \underline{i_{B3}} \end{cases}$$

$$\underline{Z_{11}} = \underline{Z_1} + \underline{Z_2} = 5+3j$$

$$\underline{Z_{12}} = -\underline{Z_2} = 2(1-j)$$

$$\underline{E_1}' = \underline{E_1} = -50\sqrt{2}(1+j)$$

$$(5+3j) \underline{i_1}' + 2(1-j) \cdot 5\sqrt{2}(1+j) = -50\sqrt{2}(1+j)$$

$$(5+3j) \underline{i_1}' = -50\sqrt{2}(1+j) - 10\sqrt{2} \cdot (-2j)$$

$$(5+3j) \underline{i_1}' = -50\sqrt{2} - 30\sqrt{2}j$$

$$(5+3j) \underline{i_1}' = -10\sqrt{2}(5+3j)$$

$$\underline{i_1}' = -\frac{10\sqrt{2}(5+3j)}{5+3j} = -10\sqrt{2}$$

$$i_1 = +\underline{i_1}' = -10\sqrt{2} = 10\sqrt{2} e^{j\pi}$$

$$i_2 = \underline{i_1}' + \underline{i_2}' = -10\sqrt{2} + 5\sqrt{2}(1-j) \\ = +5\sqrt{2}(-1+j) = 10 e^{j \frac{3\pi}{4}}$$

$$-2 \sim 2 \cdot \frac{5\sqrt{2}}{2} (-1+j) = 10 \left( -\frac{\sqrt{2}}{2} + \frac{\sqrt{2}}{2}j \right)$$

$$\underline{z}_2 \underline{i}_2 = \underline{U}_{B3}$$

$$\underline{U}_{B3} = 2(1-j) \cdot 5\sqrt{2}(-1-j) = -10\sqrt{2} \cdot 2 = -20\sqrt{2} = 20\sqrt{2} \cdot e^{j\pi}$$

$$|U_{B3}| = 20\sqrt{2}$$

$$U_{B3,\max} = U_{B3} \cdot \sqrt{2} = 40$$

$$U_{B3}(t) = 40 \sin(100t + \pi)$$

$$i_1(t) = 20 \sin(100t + \pi)$$

$$i_2(t) = 10\sqrt{2} \sin(100t + \frac{\pi}{4})$$

Potential Node

$$\begin{cases} Y_{11} \underline{V}_1 = \underline{I}_{NC1} \\ \underline{V}_2 = 0 \end{cases}$$

$$Y_{11} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$\underline{I}_{NC1} = \frac{\underline{E}_1}{Z_1} + \underline{I}_{B3}$$

$$\begin{aligned} \underline{V}_1 - \underline{V}_2 &\Rightarrow -\underline{Z}_1 \underline{i}_1 + \underline{E}_1 \\ &\downarrow \\ &\underline{Z}_2 \underline{i}_2 \\ &\downarrow \\ &-\underline{U}_{B3} \end{aligned}$$


$$\underline{S} = P + jQ$$

$$\begin{aligned} \underline{S}_{gen.} &= \underline{E}_1 \underline{i}_1^* + \underline{U}_{B3} \cdot \underline{i}_{B3}^* = -50\sqrt{2}(1+j) \cdot (-10\sqrt{2}) + (-20\sqrt{2}) \cdot 5\sqrt{2}(1+j) \\ &= 1000 + 1000j - 200 - 200j = 800(1+j) \end{aligned}$$

$$P = 800 \text{ kW}$$

$$Q = 800 \text{ VAR}$$
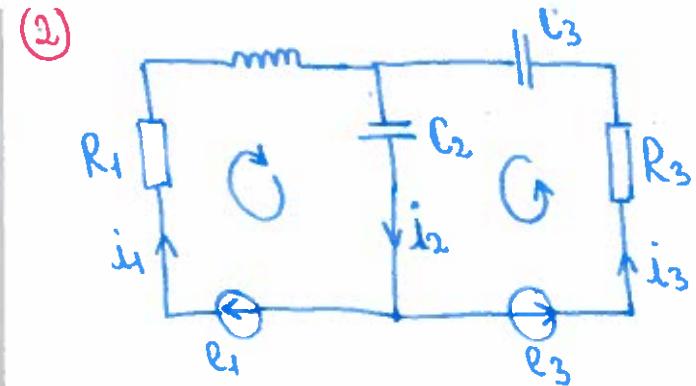
$$\begin{aligned} \underline{S}_{rec} &= \underline{Z}_1 \cdot \underline{i}_1^2 + \underline{Z}_2 \cdot \underline{i}_2^2 = (3+5j) \cdot 200 + 2(1-j) \cdot 100 \\ &= 800 + 800j \end{aligned}$$



$$e_1(t) = e_3(t) = 120 \sin(100t + \frac{\pi}{4})$$

$$R_1 = 2\Omega \quad R_3 = 1\Omega$$

$$L_1 = 40 \text{ mH}$$

$$C_2 = 5 \text{ mF}$$

$$C_3 = \frac{10}{3} \text{ mF}$$

$$\underline{Z}_1 =$$

$$\underline{Z}_2 =$$

$$\underline{Z}_3 =$$

$$\frac{i_1}{i_2} =$$

$$\underline{E}_1 = 60(1+j)$$

$$\underline{E}_3 = 60(1+j)$$

$$K_I \quad i_2(t) = i_1(t) + i_3(t)$$

$$KII \quad i_1 R_1 + L_1 \frac{di_1}{dt} + \frac{1}{C_2} \int i_2 dt = e_1$$

$$i_3 R_3 + \frac{1}{C_3} \int i_3 dt + \frac{1}{C_2} \int i_2 dt = e_3$$

$$\begin{cases} \underline{i}_2 = \underline{i}_1 + \underline{i}_3 \\ \underline{Z}_1 \underline{i}_1 + \underline{Z}_2 \underline{i}_2 = \underline{E}_1 \\ \underline{Z}_3 \underline{i}_3 + \underline{Z}_2 \underline{i}_2 = \underline{E}_2 \end{cases}$$


$$\underline{Z}_1 = R_1 + j\omega L_1 = 2 + j \cdot 100 \cdot 40 \cdot 10^{-3} = 2(1+2j)$$

$$\underline{Z}_2 = -j \frac{1}{\omega C_2} = -j \cdot \frac{1}{100 \cdot 5 \cdot 10^{-3}} = -2j$$

$$\underline{Z}_3 = R_3 - j \frac{1}{\omega C_3} = 1 - j \frac{1}{100 - \frac{10}{3} \cdot 10^{-3}} = 1-3j$$

$$\underline{E}_1 = \underline{E}_3 = \underline{E}_1 \cdot e^{j\frac{\pi}{4}} = 60\sqrt{2} \cdot e^{j\frac{\pi}{4}} = 60\sqrt{2} \left( \cos \frac{\pi}{4} + j \sin \frac{\pi}{4} \right) = 60(1+j)$$
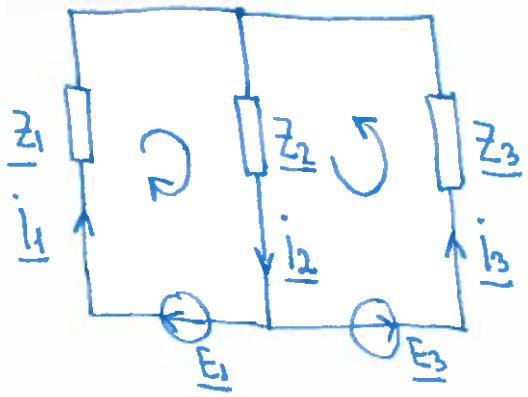
$$E_1 = \frac{120\sqrt{2}}{2} = 60\sqrt{2}$$



$$\left\{ \begin{array}{l} i_3 = i_2 - i_1 \\ 2(1+2j) \cdot i_1 + (-2j) \cdot i_2 = 60(1+j) \mid \cdot (1-5j) \\ (-1+3j) \cdot i_1 + (1-5j) i_2 = 60(1+j) \mid \cdot -2j \end{array} \right.$$

$$\Rightarrow [2(1+2j)(1-5j) + 2j(-1+3j)] i_1 = 60(1+j)(1-5j+2j)$$

$$(1-5j+2j+10-j-3) i_1 = 30(-1-3j+j+3)$$

$$4(2-j) i_1 = 60(2-j) \Rightarrow i_1 = 15A$$

~~$$30 + 60j - 2j \cdot i_2 = 60 + 60j \Rightarrow i_2 = 30(1+j) = 30j$$~~

$$i_3 = 15j - 15$$

$$i_1 = 15 = 15 e^{j0} \Rightarrow i_1(t) = 15\sqrt{2} \sin(100t)$$

$$i_2 = 15j = 15 e^{j\frac{\pi}{2}}$$

$$i_3 = 15(-1+j) = 15\sqrt{2} \left( -\frac{\sqrt{2}}{2} + \frac{\sqrt{2}}{2} j \right) = 15\sqrt{2} e^{j\frac{3\pi}{4}}$$

$$i_3(t) = 30 \sin(100t + \frac{3\pi}{4})$$

$$S_{\text{geom}} = E_1 \cdot i_1^* + E_3 \cdot i_3^*$$

$$S_{\text{real}} = Z_1 i_1^2 + Z_2 i_2^2 + Z_3 i_3^2$$